

# Management and analysis of physics datasets, Part. 1

## Third Laboratory

---

Antonio Bergnoli [bergnoli@pd.infn.it](mailto:bergnoli@pd.infn.it) - Filippo Marini [filippo.marini@pd.infn.it](mailto:filippo.marini@pd.infn.it)

25/11/2020

## Laboratory Introduction

---

Mainly a recap of the last lecture

- GHDL for larger projects
- Introduce processes
- introduce sequential circuits and sensitivity list

## GHDL for Larger Projects

---

```
student@MAPD-machine : ~$ ghdl -i heartbeat.vhd # include source file in the project
student@MAPD-machine : ~$ ghdl -i heartbeat_top.vhd # include source file in the project
student@MAPD-machine : ~$ ghdl -d # check the working directory

# Library work
# Directory :
entity heartbeat
architecture behaviour of heartbeat
entity heartbeat_top
architecture str of heartbeat_top

student@MAPD-machine : ~$ ghdl -m heartbeat_top # make the selected entity (usually the top)
analyze heartbeat_top.vhd
analyze heartbeat.vhd
elaborate heartbeat_top

student@MAPD-machine : ~$ ghdl -r heartbeat_top --wave=wave.ghw --stop-time=1us # run the simulation

./heartbeat_top : info : simulation stopped by --stop-time @1us

student@MAPD-machine : ~$ gtkwave wave.ghw #inspect the result (waveform)
```

**Multiplexer, doubts?**

---

# Multiplexer, doubts?

```
MUX2
library IEEE;
use IEEE.std_logic_1164.all;
entity mux2 is
  port(
    a1 : in  std_logic_vector(2 downto 0);
    a2 : in  std_logic_vector(2 downto 0);
    sel : in  std_logic;
    b   : out std_logic_vector(2 downto 0));
end mux2;
architecture rtl of mux2 is
begin
  p_mux : process(a1, a2, sel)
  begin
    case sel is
      when '0'   => b <= a1;
      when '1'   => b <= a2;
      when others => b <= "000";
    end case;
  end process p_mux;
end rtl;
```

```
MUX4
  library IEEE;
  use IEEE.std_logic_1164.all;
  entity mux4 is
    port(
      a1, a2, a3, a4 : in  std_logic_vector(2 downto 0);
      sel             : in  std_logic_vector(1 downto 0);
      b               : out std_logic_vector(2 downto 0));
  end mux4;
  architecture rtl of mux4 is
    component mux2 is
      port (
        a1, a2 : in  std_logic_vector(2 downto 0);
        sel    : in  std_logic;
        b      : out std_logic_vector(2 downto 0));
    end component mux2;
    signal muxA_out, muxB_out : std_logic_vector(2 downto 0);
  begin
    muxA : mux2
      port map ( a1 => a1, a2 => a2,
                 sel => sel(0),
                 b   => muxA_out);
    muxB : mux2
      port map ( a1 => a3, a2 => a4,
                 sel => sel(0),
                 b   => muxB_out);
    muxOut : mux2
      port map ( a1 => muxA_out, a2 => muxB_out,
                 sel => sel(1),
                 b   => b);
  end rtl;
```

## Sequential circuits

---



- Statements are executed one after the other sequentially, in order
- Processes are used to describe sequential behavior
- All processes in an architecture behave concurrently

The process includes the “sensitivity list”, which is a set of signals on which any change triggers the process itself

- Process runs when any of the signals in the sensitivity list changes
- A process with a sensitivity list must not contain any “wait” statement
- The sensitivity list can only include signals and input ports
- The execution of a process consists in the execution of its whole sequence of statements

```
library ieee;
use ieee.std_logic_1164.all;
entity process_ex is
    port (
        a : in  std_logic;
        b : in  std_logic;
        c : in  std_logic;
        y : out std_logic
    );
end entity process_ex;
architecture rtl of process_ex is
    signal x : std_logic;
begin -- architecture rtl
    process (a, b, c, x)
    begin
        x <= (a and b) or c;
        y <= x;
    end process;
end architecture rtl;
```

# Sequential Clocked Process

- Generates synchronous logic circuits
- All signals are evaluated at the rising edge of the clock, no need to add other signals on the sensitivity list

```
library ieee;
use ieee.std_logic_1164.all;
entity dff is
    port (
        clk : in  std_logic;
        rst : in  std_logic;
        d   : in  std_logic;
        q   : out std_logic);
end entity dff;
architecture rtl of dff is
begin -- architecture rtl
    flipflop : process (clk) is
    begin -- process flipflop
        if rising_edge(clk) then -- rising clock edge
            if rst = '0' then
                q <= '0';
            else
                q <= d;
            end if;
        end if;
    end process flipflop;
end architecture rtl;
```

## Classwork

---

## Suggested exercise

- Build a testbench for the D Flip-Flop
- Design the architecture of a Toggle Flip-Flop
- Build a testbench to check its behavior

 


Figure 1: Toggle Flip-Flop Model

$T$	$Q_n$	$Q_{n+1}$
0	0	0
0	1	1
1	0	1
1	1	0

Figure 2: Toggle Flip-Flop Truth Table