

Management and Analysis of Physical Datasets – I

a.a. 2019-20

FPGA and VHDL

G.Collazuol


Overview

- 1) Introduction to FPGA and VHDL
- 2) VHDL Language elements
- 3) Concurrent vs Sequential Statements
- 4) Some relevant examples
- 5) Finite State Machines
- 6) Buses
- 7) Memories


Introduction to FPGA

Old ways of implementing digital circuits

 - ◆ Discrete logic – based on gates or small packages containing small digital building blocks (at most a 1-bit adder)
- ◆ De Morgan's theorem – theoretically we only need 2-input NAND or NOR gates to build anything
- ◆ Tedious, expensive, slow, prone to wiring errors




Old digital integrated circuits

 


- ◆ Rows of gates – often identical in structure
- ◆ Connected to form customer specific circuits
- ◆ Can be full-custom (i.e. completely fabricated from scratch for a given design)
- ◆ Can be semi-custom (i.e. customisation on the metal layers only)
- ◆ Once fabricated, the design is fixed

Modern custom digital IC

 
- ◆ Intel Core i7
- ◆ $> \frac{3}{4}$ billion trans.
- ◆ Very expensive to design
- ◆ Very expensive to manufacture
- ◆ Not viable unless the market is very large



Programmable Logic Devices

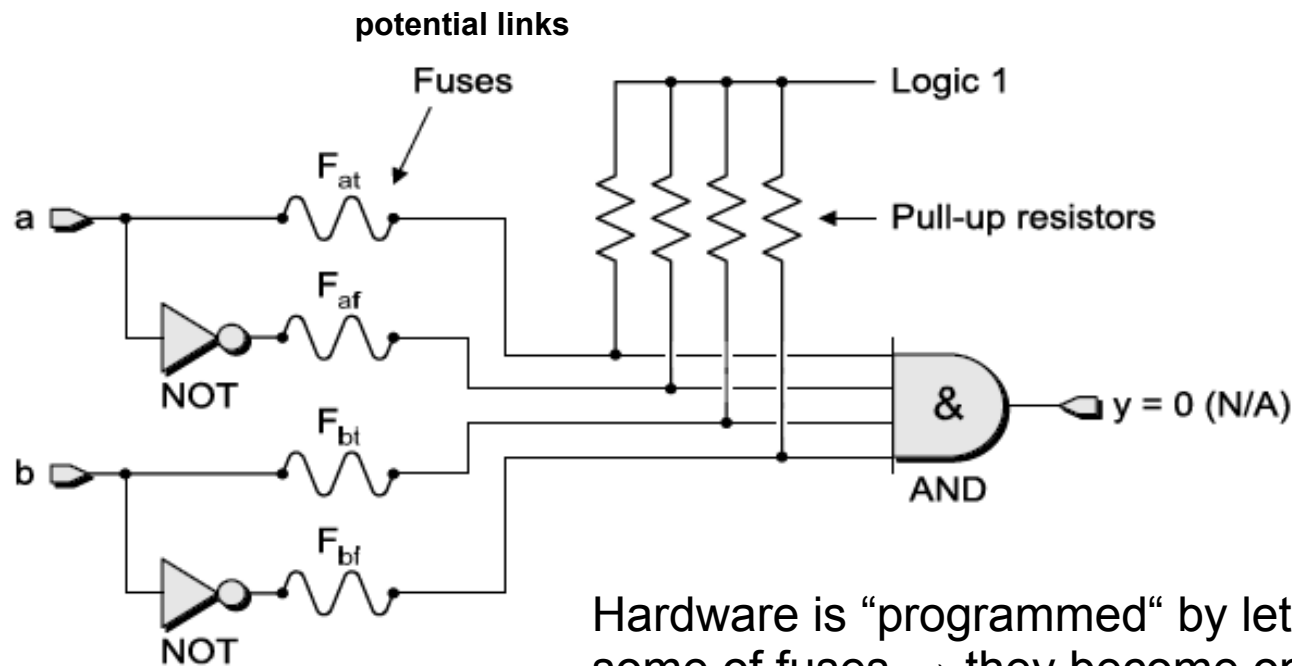

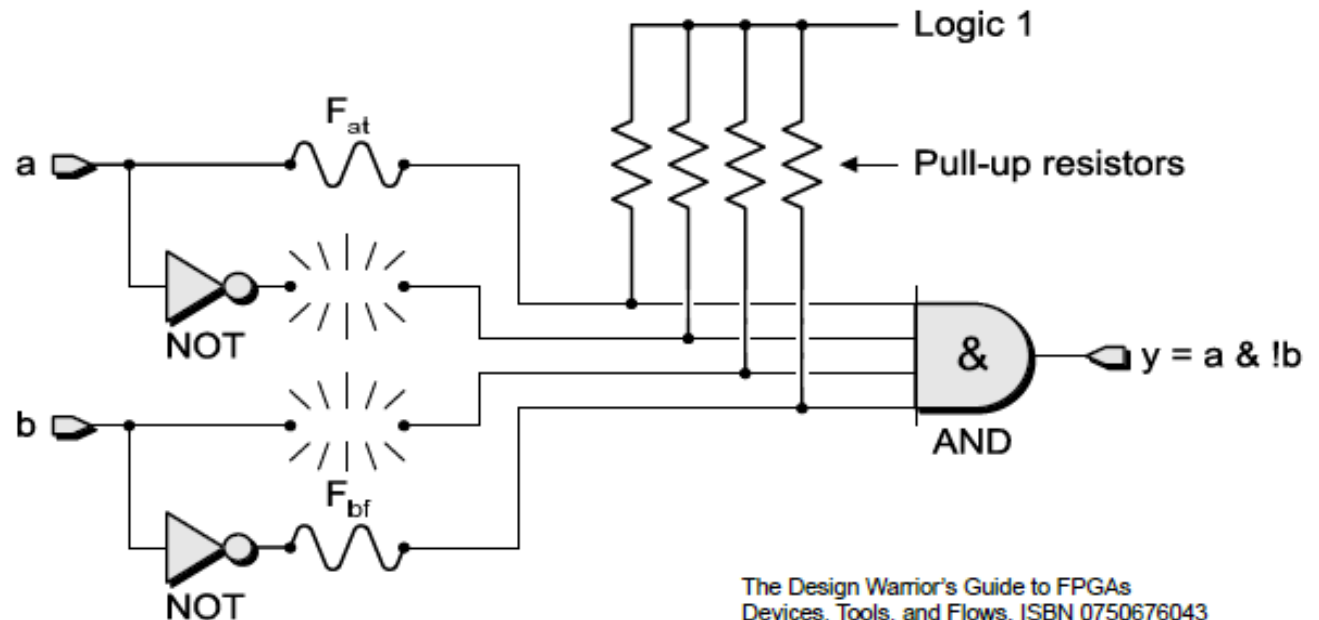
Hardware is “programmed” by letting flow high current through some of fuses → they become open-circuits



Programmable Logic Arrays

A Programmable Logic Array (PLA) is a type of logic device that can be programmed to implement various kinds of combinational logic circuits. The device has a number of **AND** and **OR** gates which are linked together to give output or further combined with more gates or logic circuits

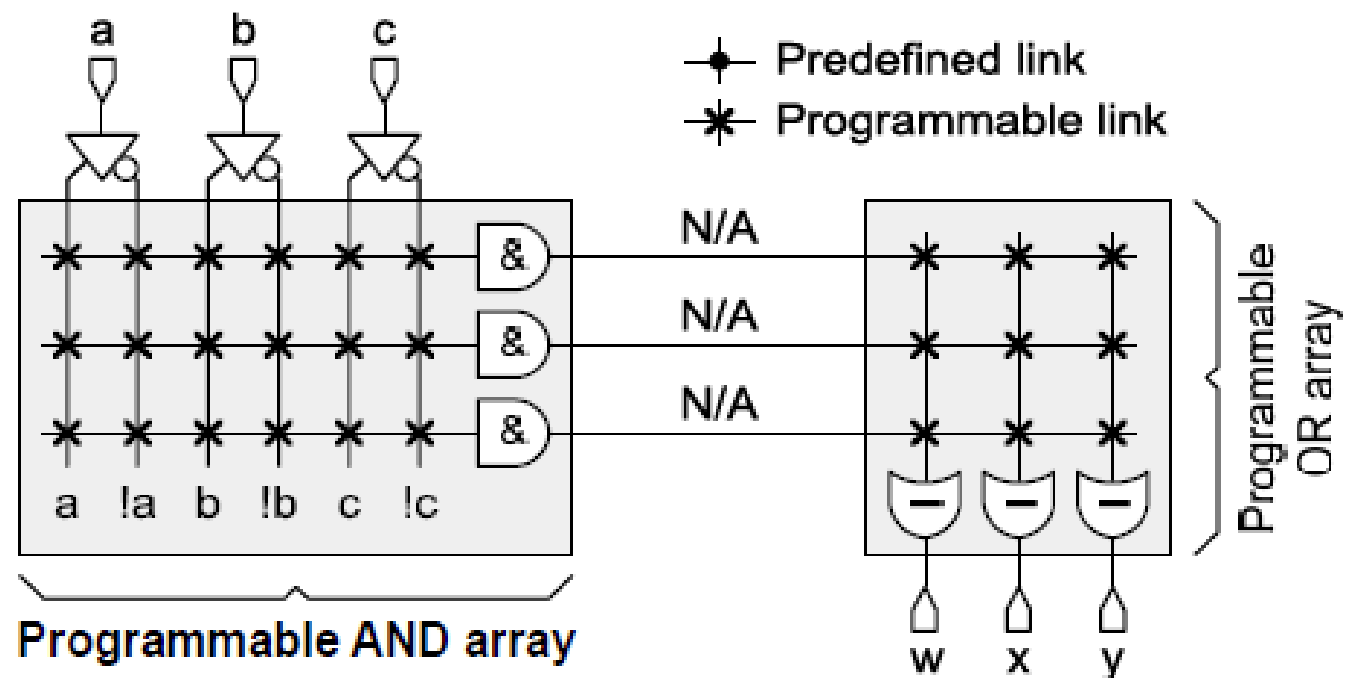Reminder:
combinational
logic block
synthesis




On a PLA is different logical functions can be combined as a **sum-of-product** or **product-of-sum** form: a PLA having N input buffers and M output buffers consists of 2N AND gates and M OR gates, each with programmable inputs from all of the AND gates.

PLAs have widely been acknowledged as compact and space-efficient solutions for many complicated circuits, especially in feedback and control systems where a number of factor variables must be involved for efficient functioning of the system


Complex Programmable Logic Device

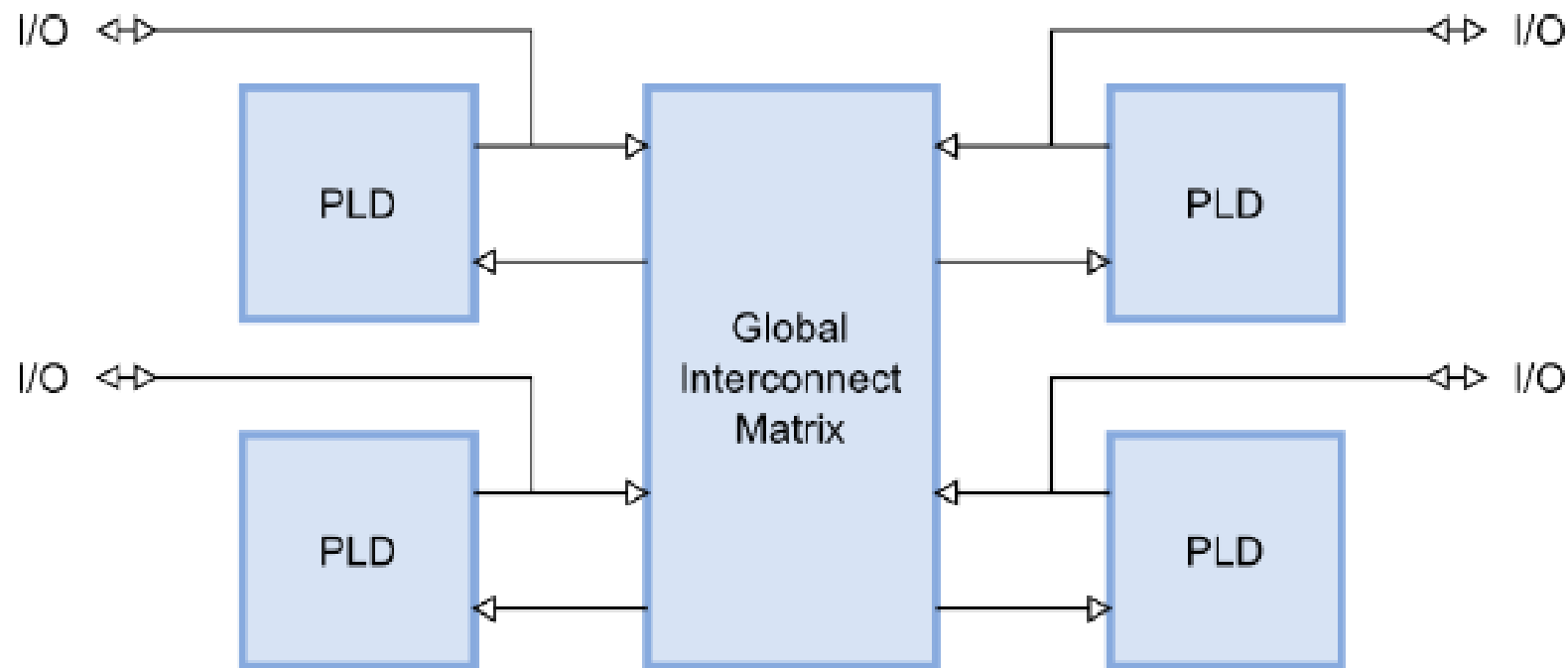A CPLD contains a bunch of PLD blocks like the one shown above, but their inputs and outputs are connected together by a *global interconnection matrix*. So a CPLD has two levels of programmability: each PLD block can be programmed, and then the interconnections between the PLDs can be programmed.




Field Programmable Gate Arrays - FPGA

An FPGA takes a different approach. It has a bunch of simple, *configurable logic blocks* (CLBs) interspersed within a *switching matrix* that can rearrange the interconnections between the them. Each logic block is individually programmed to perform a logic function (such as AND, OR, XOR, etc.) and then the switches are programmed to connect the blocks so that the complete logic functions are implemented.

 



Example of CLB

 

  - 1) Look Up Table (LUT)
→ any combinatory function (3 input)
- 2) flip-flop (FF)
→ 1-bit memory
- 3) additional input
→ to combine large combinatory functions through multiplexer (MUX)


FPGA – Programmable Routing

- ◆ Between rows and columns of logic blocks are wiring channels
- ◆ These are programmable – a logic block pin can be connected to one of many wiring tracks through a programmable switch
- ◆ Xilinx FPGAs have dedicated switch block circuits for routing (more flexible)
- ◆ Each wire segment can be connected in one of many ways:




FPGA – Programming

- ◆ Programming an FPGA is NOT the same as programming a microprocessor
- ◆ We download a **BITSTREAM** (not a program) to an FPGA
- ◆ Programming an FPGA is known as **CONFIGURATION**
- ◆ All LUTs are configured using the BITSTREAM so that they contain the correct values to implement the Boolean logic
- ◆ Shown here is a typical implementation of a 4-LUT circuit
 - ABCD are the FOUR inputs
 - There is four level of 2-to-1 multiplexer circuits
 - The 16-inputs to the mux tree determine the Boolean function to be implemented as in a truth-table
 - These 16 binary values are stored in registers (DFF)
 - Configuration = setting the 16 registers to 1 or 0

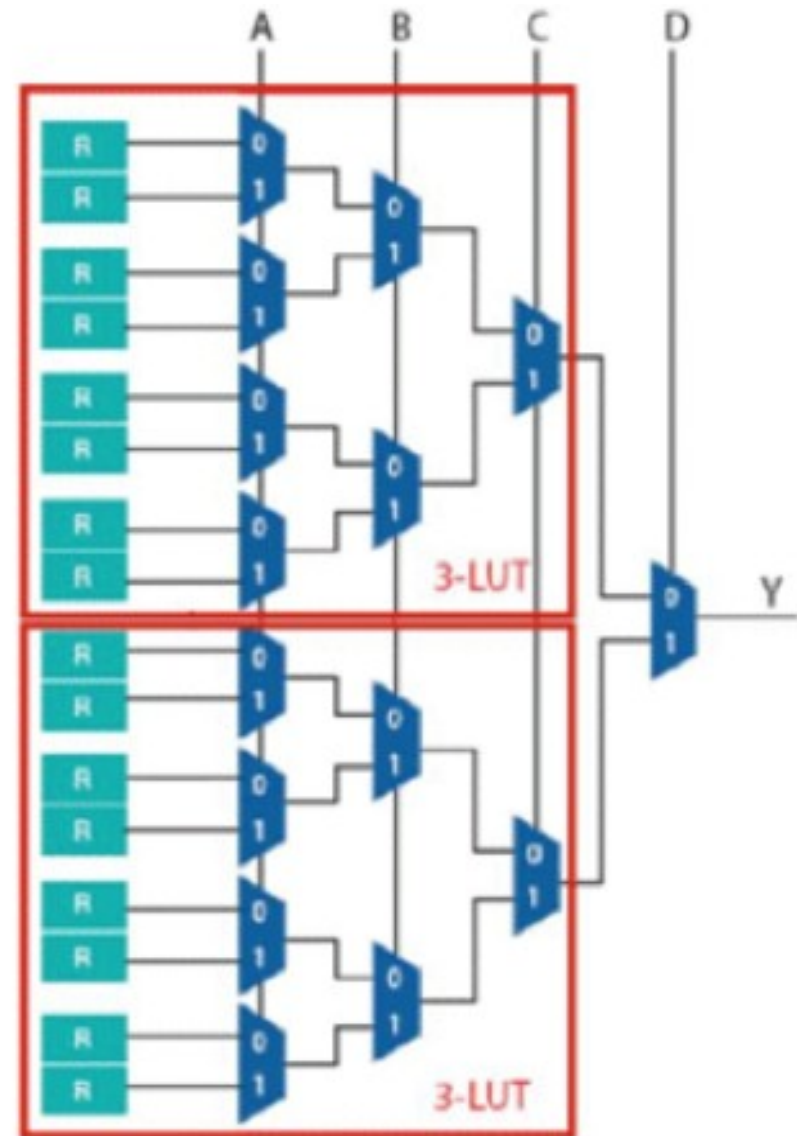


FPGA – Programming

 - ◆ At each interconnect site, there is a transistor switch which is default OFF (not conducting)
- ◆ Each switch is controlled by the output of a 1-bit configuration register
- ◆ Configuring the routing is simply to put a '1' or '0' in this register to control the routing switches
- ◆ Bitstream is either stored on local flash memory or download via a computer
- ◆ Configuration happens on power-up




FPGA – Project flow

 

Note: Spice netlist

→ text-based representation of a circuit

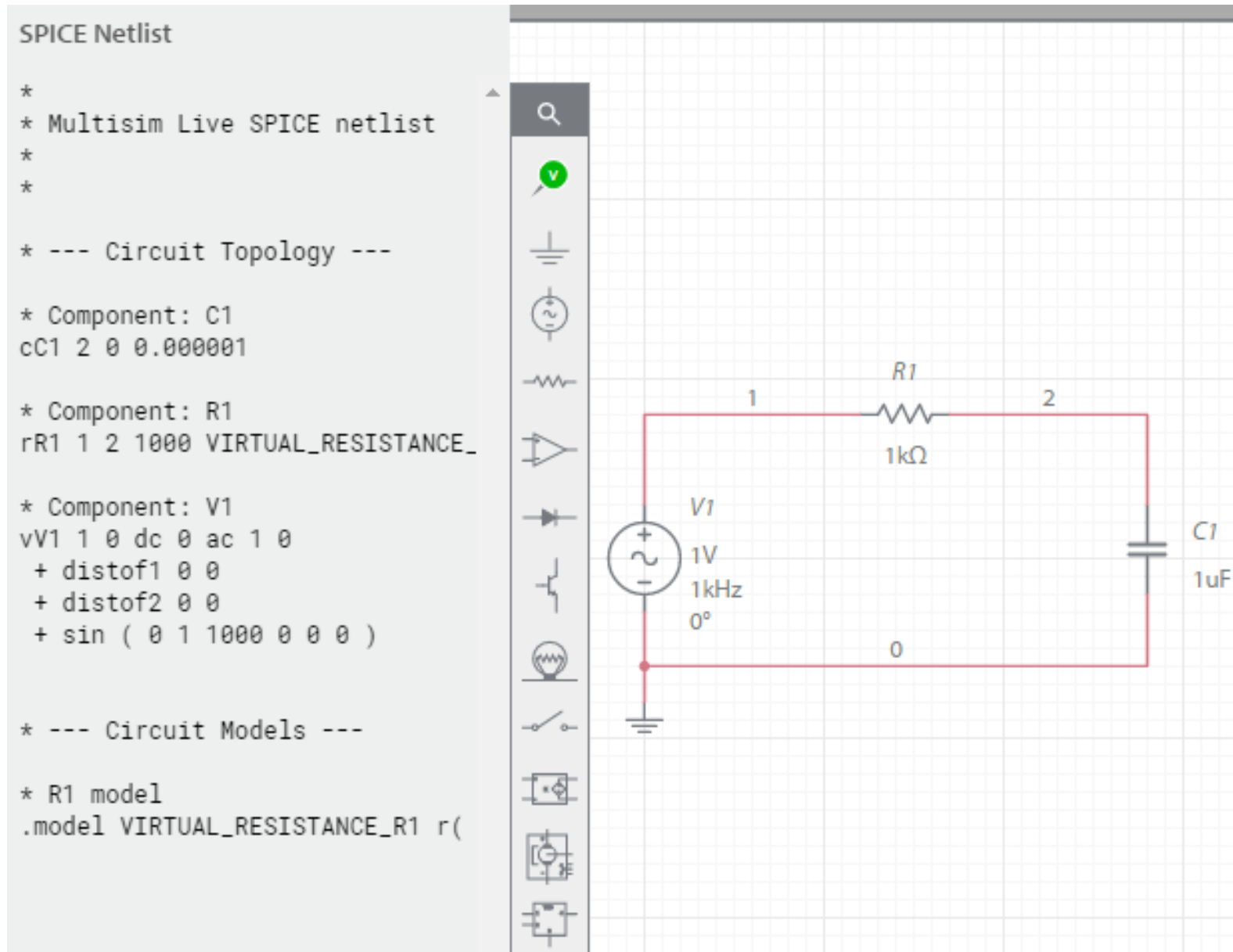

Introduction to VHDL

Introduction to HDL

Circuit description in the early '70-ies



Description of the circuit with **Spice** netlist (**component** level)

Complete circuit characterization:

- Real models of the components
- extraction of Parasitic effects



Simulazione

  


```
CMOS Inverter
.lib 'models25.txt' TT
mn1 VSS IN OUT VSS nmos l=0.24u w=0.72u
mp1 VDD IN OUT VDD pmos l=0.24u w=0.72u
cLoad OUT VSS 50fF
vVDD VDD 0 2.5
vVSS VSS 0 0
vIN IN 0 pulse( 0 2.5 100ps 100ps 100ps 2ns 4ns )
.dc vIN start=0 stop=2.5 step=0.01
.tran 1ps 8ns
.option post
.end
```

Introduction to HDL

Circuit description in the '80-ies

Description of the circuit blocks (schematic level)

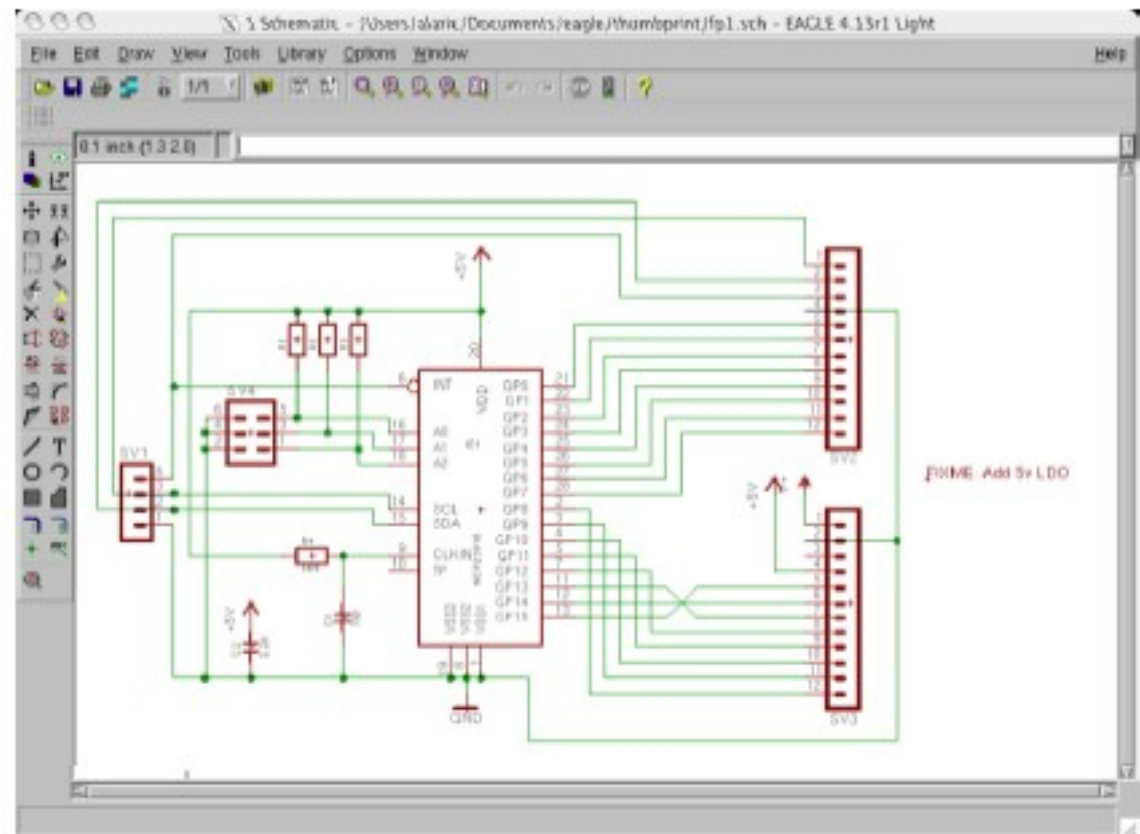- CAD → short development time
- use of pre-built Libraries
- no need of full project for extracting the parasitic effects



Introduction to HDL

Circuit description in the '90-ies

Description of the circuit with **High Level Description Language** (functional level)

- use **functional blocks** described in detail
 - allows for simulations with various level of accuracy
 - synthesis
- + CAD
+ Libraries
+ ...

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use ieee.std_logic_arith.all;
entity ALU is
    port( A: in std_logic_vector(1 downto 0);
          B: in std_logic_vector(1 downto 0);
          Sel: in std_logic_vector(1 downto 0);
          Res: out std_logic_vector(1 downto 0));
end ALU;
architecture behv of ALU is begin
    process(A,B,Sel) begin
        case Sel is
            when "00" => Res <= A + B;
            when "01" => Res <= A + (not B) + 1;
            when "10" => Res <= A and B;
            when "11" => Res <= A or B;
            when others => Res <= "XX";
        end case;
    end process;
end behv;
```

Introduction to HDL

Two languages developed ad hoc

- **VHDL** (Very High speed integrated circuit – HDL)
 - developed for the US government / military
 - made standard by IEEE
 - nowadays widespread in EU industry
- **VERILOG**
 - developed by the electronics industry
 - made standard by IEEE
 - nowadays widespread in US industry

Other languages based on existing languages

- **System-C**
- System-VHDL, System-Verilog, etc...

a bit of VHDL history...

VHDL was originally developed at the behest of the US Department of Defense in order to **document the behavior of the ASICs that supplier companies** were including in equipment.
→ VHDL was developed as an **alternative to huge, complex manuals** which were subject to implementation-specific details

The idea of being able to **simulate this documentation** was so obviously attractive that logic simulators were developed that could read the VHDL files.
→ The next step was the **development of logic synthesis** tools that read the VHDL, and output a definition of the physical implementation of the circuit

Due to the Department of Defense requiring as much of the syntax as possible to be based on **Ada**, in order to avoid re-inventing concepts that had already been thoroughly tested in the development of Ada, **VHDL borrows heavily from the Ada** programming language in both concepts and syntax

The initial version of VHDL, designed to IEEE standard 1076-1987, included a **wide range of data types**, including numerical (integer and real), logical (bit and boolean), character and time, plus arrays of bit called `bit_vector` and of character called `string`...

... long history up to the most recent VHDL standard IEEE 1076-2008 published in January 2009

Introduction to VHDL

How can modern VHDL describe a circuit ? Choices are:

1. Schematic capture (graphical mode)

- draw the circuit blocks → instantiate the logical components
- synthesis tool → maps the circuit realized within the device

2. Hardware Description Language (code list mode)

- describe by appropriate language the operation of our system
- synthesis tool → translates the code into the component's structures

Mix of the two modes also possible ! → Mixed Mode

Introduction to VHDL

Looks like a “normal” programming language (typically C):

- various types of data and objects (constants, variables, expressions)
- arithmetic / logical operators, sequential instructions (if, while, for ...)
- functions, sub-programs

Implement specific elements to efficiently model **hardware blocks**:

- allow to define components and instantiate them in a **hierarchical structure**
- support the representation of **concurrent events**
(ie, operations that are **not always activated in the same temporal order**)

Allow to describe the system at **different levels of abstraction**

- from the highest level (system) up to the logical level (network of logic gates)
- traditional representation systems usually are specialized for one or two levels:
 - block diagrams \Rightarrow system / data-flow;
 - logical schemes \Rightarrow logical level;
 - electric schemes \Rightarrow electrical level;

VHDL description modes

Behavioral

- system **functionality** description (by algorithms, conditions, loops)
regardless of signals flow and implementation at elementary cells level
- correct operations **sequence** BUT **no time information**


Register Transfer Level (RTL or Data-Flow)

- description of the system in terms of **signal flow among registers**
including connections (registers, combinational logic, bus, control units...)
- assignment of **operations to a given clock cycle**

Structural

- description of the system as a **network of elementary components**
(described in behavioral level)
- detailed **analysis of delay times** possible


VHDL description modes

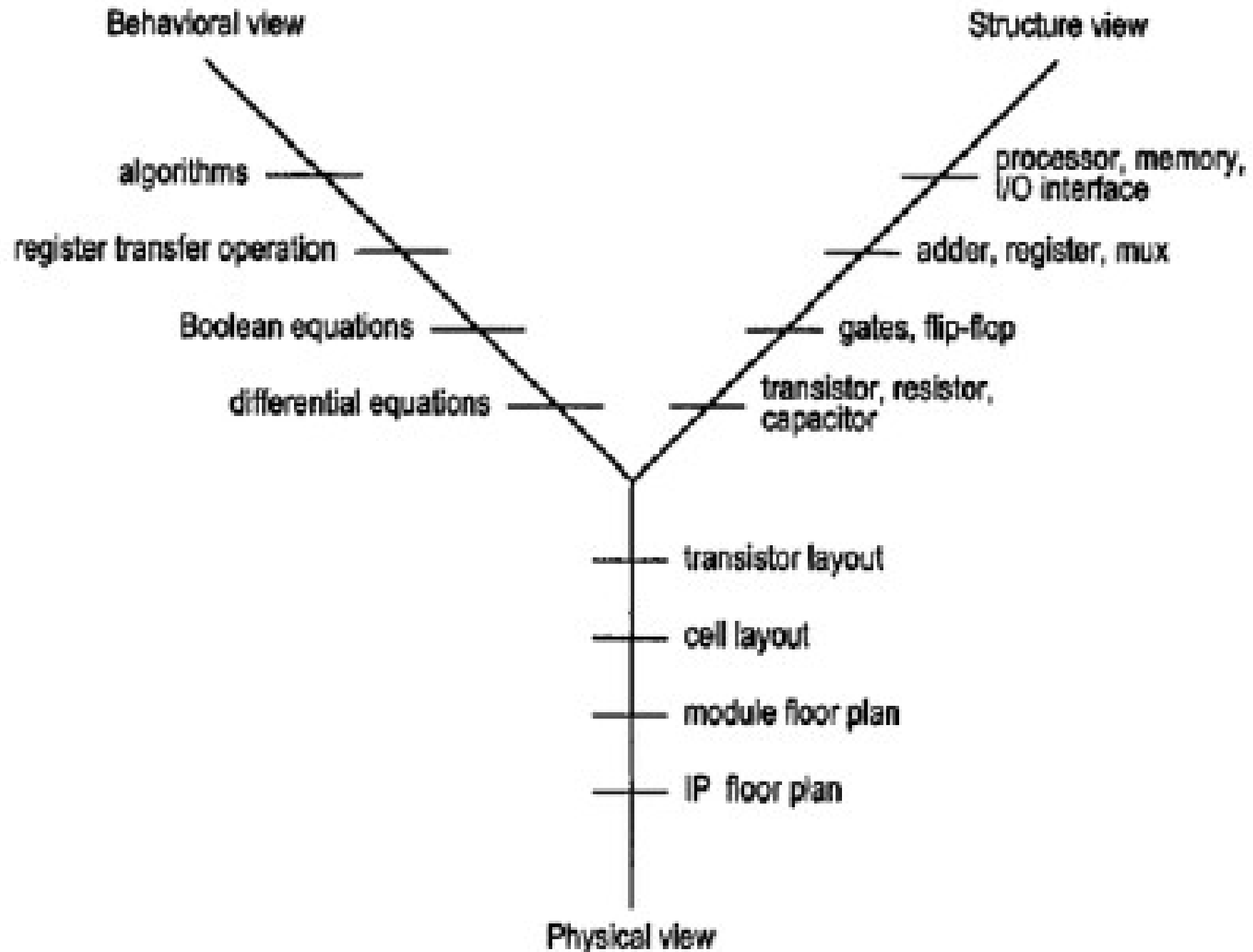

VHDL project flow

- VHDL supports all levels of the design flow
development → simulation → synthesis → testing + documentation
- allows **description independent** of the implementation technology
⇒ portability of the project from one technology to another
- allows **system event simulation**
validation of very complex systems
- allows **automatic synthesis**
 - from RTL to cell netlist (standard)
 - from behavioral to RTL (not standard)

VHDL project flow (Xilinx)

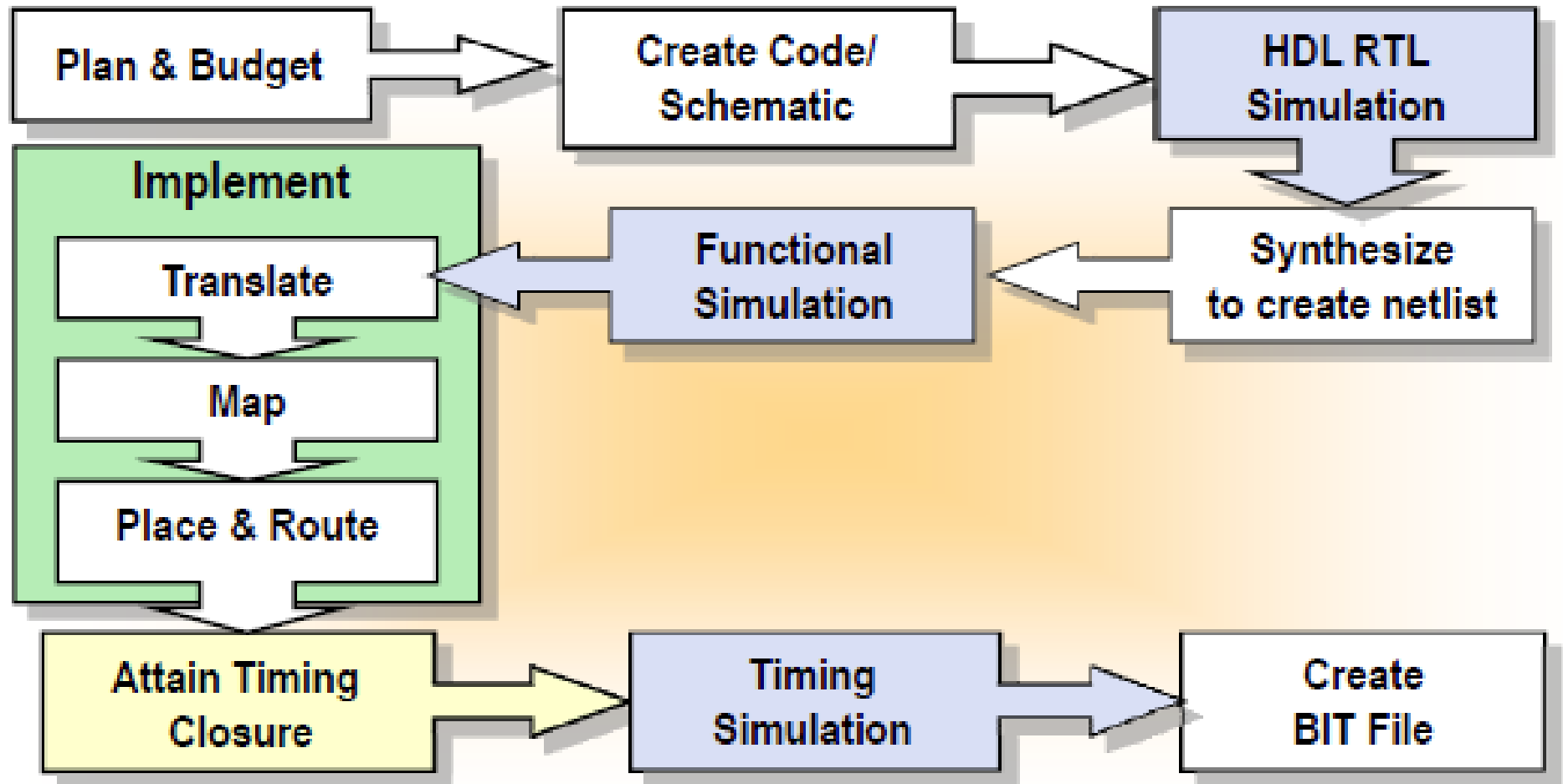

VHDL in practice...

Good practice rules:

- write your code considering that **instructions** are **translated** into **circuits**
- which are processing / reacting to real **signals** or **events**

I - VHDL basics


1. entity and architecture
2. signals and processes
3. simulation
4. synthesis

1 - VHDL description basics

Entity & Architecture

The description of a module in VHDL is made up of **two main elements**:

 - an interface (**entity**)
→ defines the I / O terminals and the name of the circuit
- one or more implementations (**architecture**)
→ describe the behavior or the internal structure of the circuit



1 - VHDL description basics: Entity



ENTITY


It defines the (black) box:

- name
- terminals w/ direction (in/out)
- data type

```
entity FULL_ADDER is
    port (A, B, CI: in bit;
          CO, S: out bit);
end FULL_ADDER;

architecture BHV of FULL_ADDER is
    signal P, G: bit;
begin
    P <= A xor B;
    G <= A and B;
    S <= P xor CI;
    CO <= (P and CI) or G;
end BHV;
```

 1 - VHDL description basics: Architecture



ARCHITECTURE

Defines the box functionality:

architecture ... of ... is

Includes the following parts:

- **Declaration** (before **begin**)
decl. internal signals/variables
- **Assertions** (**begin** to **end**)
describes circuit behaviour by using
 - **operations** among signals (internal and/or I/O) and
 - **assignement** (**<=**)

```
entity FULL_ADDER is
    port (A, B, CI: in bit;
          CO, S: out bit);
end FULL_ADDER;

architecture BHV of FULL_ADDER is
    signal P, G: bit;
begin
    P <= A xor B;
    G <= A and B;
    S <= P xor CI;
    CO <= (P and CI) or G;
end BHV;
```

Note: these are not “instructions” to be executed once: they are **descriptions of operations that are always ready** to be activated, into the described hardware

2 - VHDL main model elements:

signal & process

Main elements of a VHDL model: **signals** and **processes**

- a **process** is a block of code that describes the operation of a logic module (**sequential** or **combinatorial**)
- different **processes communicate** with each other through **signals**
- a **process is activated** and executes its function in **response to an event** ie, to a **change in value of one of the signals to which it is sensitive** (indicated in an appropriate list appropriate)
- in some cases, the function represented by a process can be described with one concurrent **assignment** simple or conditioned to a signal

```
architecture BHV2 of AOI is
begin
  Z <= C nor (A and B);
end BHV;
```

simple
assignment

```
architecture BHV3 of AOI is
begin
  Z <= '0' when C = '1' else
    A and B;
end BHV;
```

concurrent
condition

```
architecture BHV1 of AOI is
begin
  process(A,B,C) begin
    if C = '1' then
      Z <= '0';
    else
      Z <= A nand B;
    end if;
  end process;
end BHV;
```

sequential
condition

2 - VHDL main model elements:

signals

Signals are data structures able to **represent (digital) waveforms in time**

The **signal** instruction can be **declared**

- in the **architecture** with the signal statement or
- in the clause **port** of the **entity**

```
signal P, G: bit;  
...  
P  <= A xor B;  
G  <= A and B;  
S  <= P xor CI;  
...
```

- signals are **associated** with a **type** (e.g bit) and may have an **initial value**
- in **architecture** assertive part there are
 - operations between signals (**xor**, **and**, ...) and
 - assignments (<=);operators can be primitive of the VHDL or user-defined functions and procedures
- to the left of the **assignment** sign (<=) is the **target** (which must be a signal)
to the right the **signal driver** (the input) (the output)

- the **assignment** establishes a link between its inputs (the signals contained in the driver) and its output (the target) so it is **activated only when there is an event (ie a change in value) of one of the inputs**
- consequently, the **order** with which assignments are written inside of the architecture **does not matter**

3 - VHDL simulation

VHDL simulator is a program capable of applying a temporal succession of the inputs (input waveforms), and determine the time sequence of the outputs (waveform) of a circuit described by a VHDL model

It is an **event driven** simulator, whose ingredients are:

- 1) internal **model of time**;
- 2) **signals update**;
- 3) **execution** of the **processes** and the **drivers** (event processing)


Note: an **event** is the **change in the value of a signal**, to which it is associated an internal time which represents the operating time of the simulated circuit (... it is NOT the time that the computer takes to run the simulation)

3 - VHDL simulation


The simulation proceeds by jumps from one event to the next one

→ jumps along the **queue of input events**

 - 1.a each event activates the **drivers** and **processes** that are sensitive to the signal triggered the event
- 1.b the drivers calculate the new target signal value
- 1.c the new value ("transaction") is inserted in the queue of the events
→ **new transactions (potential events) inserted within the queue**
The execution of all drivers sensitive to the event causes the insertion of one or more transactions in the simulation event queue
2. when the driver execution phase is over, **the simulation jumps to the next transaction in the queue and update the value of the related signal:**
→ if the updated value is different from the previous value
we have an event → a new phase of execution of the drivers sensitive to it
→ otherwise the simulator jumps to the next transaction in the queue



3 - VHDL simulation: example

 


Elaborazione della coda degli eventi (*event processing*):

il simulatore carica la prima transazione della coda (A → 1), confronta il nuovo valore di A (1) con il vecchio (0), e, se sono diversi, inserisce un evento nella forma d'onda del segnale


```
entity FULL_ADDER is
    port (A, B, CI: in bit;
          CO, S: out bit);
end FULL_ADDER;

architecture BHV of FULL_ADDER is
    signal P, G: bit;
begin
    P <= A xor B;
    G <= A and B;
    S <= P xor CI;
    CO <= (P and CI) or G;
end BHV;
```


3 - VHDL simulation: example

 


3 - VHDL simulation: example

 

3 - VHDL simulation: example

 


3 - VHDL simulation: example

 

Elaborazione della coda degli eventi (*event processing*):

il simulatore carica la transazione successiva ($G \rightarrow 0$), confronta il nuovo valore di G (0) con il vecchio (0), e, siccome il valore di G non è cambiato, non inserisce nessun evento nella forma d'onda; i driver e i processi sensibili a G non si attivano

3 - VHDL simulation: example

 

5 ns	5 ns	5 ns	5 ns	5 ns	10 ns		
A→1	P→1	G→0	S→1	CO→0	B→1		

↑

Elaborazione della coda degli eventi (*event processing*):

il simulatore carica la transazione successiva ($S \rightarrow 1$), confronta il nuovo valore di S (1) con il vecchio (0), e inserisce il nuovo valore nella forma d'onda; non ci sono driver e/o processi sensibili a S, per cui il simulatore passa alla transazione successiva

A	0	5				
	0	1				

B	0					
	0					


P	0	5				
	0	1				

G	0					
	0					


S	0	5				
	0	1				

CO	0					
	0					


3 - VHDL simulation: example

 


3 - VHDL simulation: example

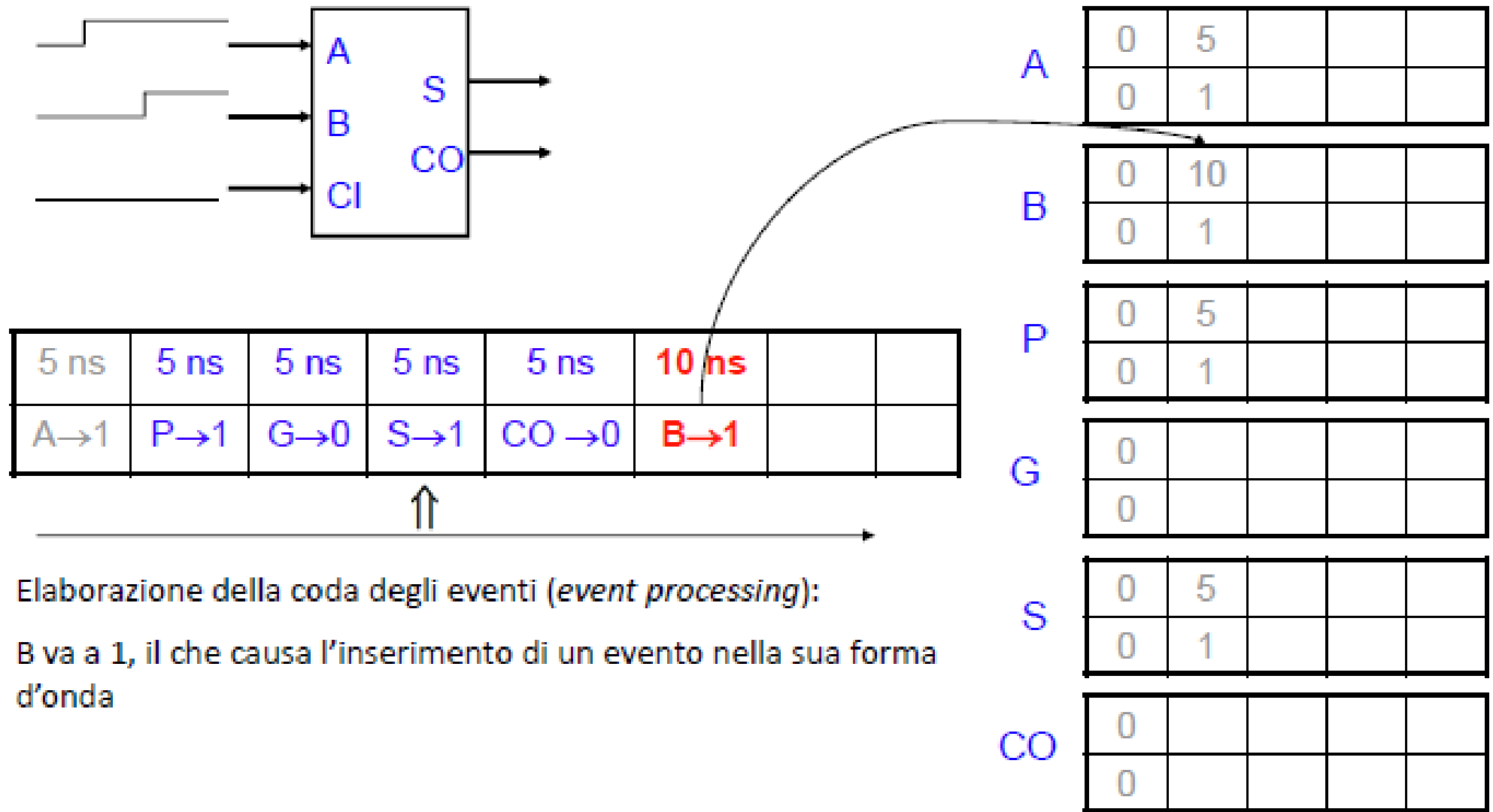

3 - VHDL simulation: example

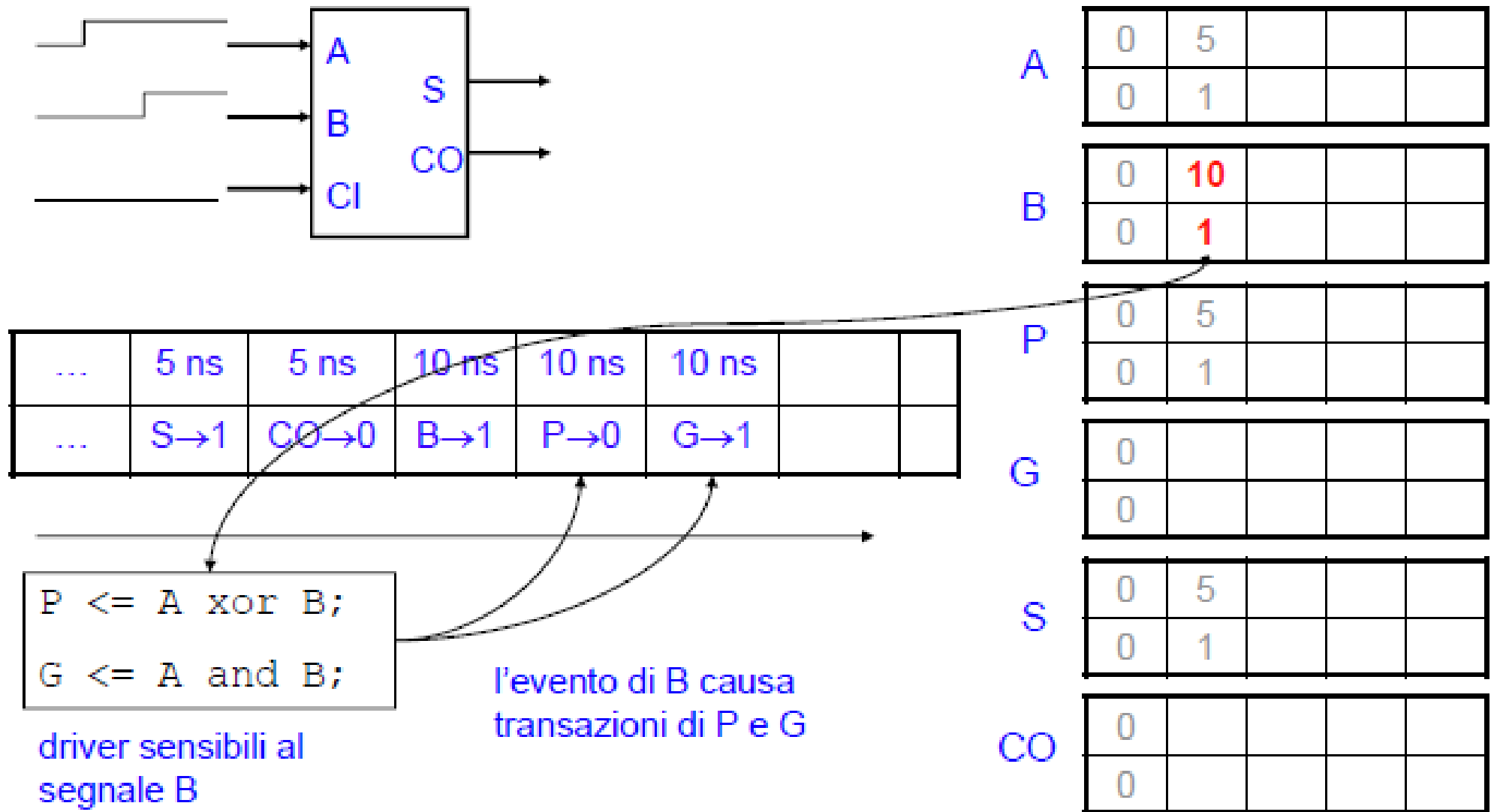

3 - VHDL simulation: example

 

...	5 ns	5 ns	10 ns	10 ns	10 ns		
...	S→1	CO→0	B→1	P→0	G→1		

↑

Elaborazione della coda degli eventi (*event processing*):

P va a 0, il che causa l'inserimento di un evento nella sua forma d'onda

A	0	5			
	0	1			

B	0	10			
	0	1			


P	0	5	10		
	0	1	0		

G	0				
	0				

S	0	5			
	0	1			

CO	0				
	0				

3 - VHDL simulation: example

 

...	10 ns	10 ns	10 ns	10 ns	10 ns		
...	B→1	P→0	G→1	S→0	CO→0		

```

S <= P xor CI;
CO <= (P and CI) or G;


```

driver sensibili al
segnale P

esecuzione dei
processi e dei
driver

A	0	5			
	0	1			
B	0	10			
	0	1			
P	0	5	10		
	0	1	0		
G	0				
	0				
S	0	5			
	0	1			
CO	0				
	0				

3 - VHDL simulation: example

 

...	10 ns	10 ns	10 ns	10 ns	10 ns		
...	B→1	P→0	G→1	S→0	CO→0		

↑

Elaborazione della coda degli eventi (*event processing*):

G va a 1, il che causa l'inserimento di un evento nella sua forma d'onda

A	0	5			
	0	1			

B	0	10			
	0	1			


P	0	5	10		
	0	1	0		

G	0	10			
	0	1			

S	0	5			
	0	1			

CO	0				
	0				

3 - VHDL simulation: example

 

...	10 ns	10 ns	10 ns	10 ns	10 ns	10 ns	
...	B→1	P→0	G→1	S→0	CO→0	CO→1	

`CO <= (P and CI) or G;`

driver sensibili al
segnale G

esecuzione dei
processi e dei
driver

A

0	5			
0	1			

B

0	10			
0	1			

P

0	5	10		
0	1	0		

G

0	10			
0	1			


S

0	5			
0	1			

CO

0				
0				

3 - VHDL simulation: example

 

...	10 ns	10 ns	10 ns	10 ns	10 ns	10 ns	
...	B→1	P→0	G→1	S→0	CO→0	CO→1	

↑↑

Elaborazione della coda degli eventi (*event processing*):

S va a 0, il che causa l'inserimento di un evento nella sua forma d'onda; non ci sono driver e/o processi sensibili a S, per cui il simulatore passa alla transazione successiva

A	0	5			
	0	1			

B	0	10			
	0	1			


P	0	5	10		
	0	1	0		

G	0	10			
	0	1			

S	0	5	10		
	0	1	0		

CO	0				
	0				

3 - VHDL simulation: example

 

...	10 ns	10 ns	10 ns	10 ns	10 ns	10 ns
...	B→1	P→0	G→1	S→0	CO→0	CO→1

↑↑


il valore di CO non è cambiato: NO evento

A	0	5			
B	0	1			
P	0	10			
G	0	1			
S	0	5	10		
CO	0	1	0		

Elaborazione della coda degli eventi (*event processing*):

CO non cambia valore, per cui non si ha un evento; il simulatore passa alla transazione successiva nella coda

3 - VHDL simulation: example

 

...	10 ns	10 ns	10 ns	10 ns	10 ns	10 ns	
...	B→1	P→0	G→1	S→0	CO→0	CO→1	




Elaborazione della coda degli eventi (*event processing*):

CO va a 1, il che causa l'inserimento di un evento nella sua forma d'onda; non ci sono driver e/o processi sensibili a CO; non ci sono altri eventi nella coda, per cui la simulazione termina

A	0	5			
	0	1			
B	0	10			
	0	1			
P	0	5	10		
	0	1	0		
G	0	10			
	0	1			
S	0	5	10		
	0	1	0		
CO	0	10			
	0	1			

3 - VHDL simulation: example #2

- suppose that initially $Q = R = S = '1'$, $Qb = '0'$,
then that at a certain moment, in the events queue, a transaction of R to '0' appears
- when the simulator arrives at the transaction, this becomes an event because the value of R changes, then the following sequence starts:
 - driver: activates D2, which is sensitive to R and
→ inserts a transaction to '1' of Qb in the queue with null delay
 - events: the simulator advances a delta time (null), meets the transaction of Qb
update its value → have an event
 - driver: the event on Qb activates D1 which inserts a transaction to '0' of Q
 - events: the simulator advances another delta, updates Q → have a new event
 - driver: the event on Q activates D2 which inserts a transaction to '1' of Qb
 - events: the simulator advances another delta, updates Qb but does not change value;
the events are over
→ the drivers D1 and D2 remain inactive until any other events on R or on S

 

cicli *delta* di durata nulla; si fermano quando non succede più niente

```
D1: Q <= S nand Qb;
```

```
D2: Qb <= R nand Q;
```

4 - VHDL synthesis

VHDL was born as a language for **description** and **simulation**:

→ the synthesis process must **interpret the language** to infer the **corresponding logic circuit**

→ not all VHDL constructs can be **synthesized**

The synthesis process (“compilation”) can be described in 3 phases:

1. **translation**: model transformed into a **network of elementary operations**
(simple combinatorial gates, MUX/DEMUX, registers)
2. **optimization**: the logical network is optimized using various algorithms to satisfy the **constraints on propagation times and minimize the area** (and/or **power**) of the circuit
3. **technological mapping**: the optimized network is transformed to be achievable with the cells contained in a technological library
(library of standard cells or cells that can be implemented on FPGA)

→ the result is a network of physically feasible cells

4 - VHDL synthesis

... not all VHDL constructs can be synthesized

```
-- File hello_world.vhd


entity hello_world is
end entity hello_world;

architecture arc of hello_world is
begin
assert false report "Hello world!" severity note;
end architecture arc;
```

4 - VHDL synthesis: example


```
entity FULL_ADDER is
  port (A, B, CI: in bit;
        CO, S: out bit);
end FULL_ADDER;

 architecture BHV of FULL_ADDER is
  signal P, S1, G, C1: bit;
begin
  P <= A xor B;
  G <= A and B;
  S1 <= P xor CI;
  C1 <= P and CI;
  S <= S1;
  CO <= C1 or G;
end BHV;
```




Model translated into intermediate format
using elementary operations and generic logics
(ie not associated with cells of a technological library)

4 - VHDL synthesis: example

 

Optimized model:

 the network was modified in order to minimize the time delay of CO



Mapped model:

the model was mapped onto a library of standard or pre-built cells

4 - VHDL synthesis: example

VHDL description of the mapped model (netlist)

→ NAND2, NAND3, XOR2 describe the I/O terminals and the connectivity of the cells used

<pre>architecture STR of FULL_ADDER is -- dichiarazione dei componenti component NAND2 port(A, B: in bit; Z: out bit); end component; component NAND3 port(A, B, C: in bit; Z: out bit); end component; component XOR2 port(A, B: in bit; Z: out bit); end component; -- connessioni interne signal X1, X2, X3, X4: bit;</pre>	<pre>begin -- gate netlist (rete di celle) G1: NAND2 port map(A => A, B => B, Z => X1); G2: NAND2 port map(A => B, B => CI, Z => X2); G3: NAND2 port map(A => CI, B => A, Z => X3); G4: NAND3 port map(A => X1, B => X2, C => X3, Z => CO); G5: XOR2 port map(A => A, B => B, Z => X4); G6: XOR2 port map(A => CI, B => X4, Z => S); end STR;</pre>
---	--

4 - VHDL synthesis: example

The netlist must be completed by associating the **components to their VHDL models**, which are contained in the **technological library** used for the synthesis (“binding” step)

<pre>configuration C1 of FULL_ADDER is begin -- binding collettivi for all: NAND2 use entity TECHLIB.NA2(BHV); for all: NAND3 use entity TECHLIB.NA3(BHV); -- binding individuali for G5: XOR2 use entity TECHLIB.XO2(BHV); for G6: XOR2 use entity TECHLIB.WXO2(BHV); end C1;</pre>	<pre>-- libreria tecnologica ... entity NA2 is generic(TP: time := 0.2ns); port(A,B: in bit; Z: out bit); end NA2; architecture BHV of NA2 is begin -- assegnazione con ritardo TP Z <= A nand B after TP; end BHV; entity NA3 is ...</pre>
--	---


Note: there are more effective ways for binding than using the **configuration**

II - VHDL language elements

1. Code anatomy – design units
2. Syntax
3. Data types
4. Object types and arrays
5. Operators and multi value logic
6. Packages and libraries → standard logic lib
7. Instructions: sequential and concurrent
→ signals vs variables
8. Procedures and Functions


... Examples

VHDL design anatomy

 

VHDL design units

- **ENTITY**: describes the interface (I / O terminals) of each module of the model
- **ARCHITECTURE**: associated with an **ENTITY**; describes what the module does
- **PACKAGE**: contains the declarations of data types, functions and procedures
- **PACKAGE BODY**: contains the definitions of the functions e procedures declared in a **PACKAGE**
- **CONFIGURATION**: defines the link between the instances of components in a structural description, and their actual implementation

 

VHDL lexicon

- VHDL does not distinguish between upper and lower case
→ **"architecture"**, **"ARCHITECTURE"** and **"aRCHiTeCtUrE"** are the same thing
- a **comment** begins with - - (double dash) and extends to the end of the line
 - Structure similar to **"//"** used in C ++
 - DOES NOT EXIST a way to interpose comments within the lines of code (in C we use **"/* ... */"**)
- an **identifier** for signals, variables, functions, ..., starts with a alphabetic character and may contain letters, numbers and the character **_**
 - Use simple names, which recall their meaning
 - Try not to use similar names for objects not related to each other
 - Do not use names of predefined identifiers, such as BIT or TIME
 - Two consecutive underscels (**__**) are not allowed
 - Names that do not comply with these rules are also allowed: it suffices to enclose them with **"\"** (Eg. **"\ 0% \$ # & __ \"**). They can start and contain any character. Distinction between uppercase and lower case... please DO NOT USE them

VHDL lexicon

- **numbers** may be integers or real (if they include a dot):

- 0 1 435_197 623E4 -- integers
- 0.0 1.0 251.436 12.3E-4 -- real numbers
- 2 # 1100_0100 # 16 # C4 # 4 # 301 # E1 -- integer 196
- 2 # 1.1111_111_111 # E + 11 16 # F.FF # E2 -- real number 4095.0

- **characters** must be enclosed in single quotes:

- 'A' 'a' '*' '1' '0'

- a **string** of characters is enclosed in double quotes:


- "string" ""

- bit strings allow you to easily specify values for vectors (**arrays**):

- B"101100110101" -- binary
- O"5465" -- octal
- X"B35" -- hexadecimal

VHDL types of data

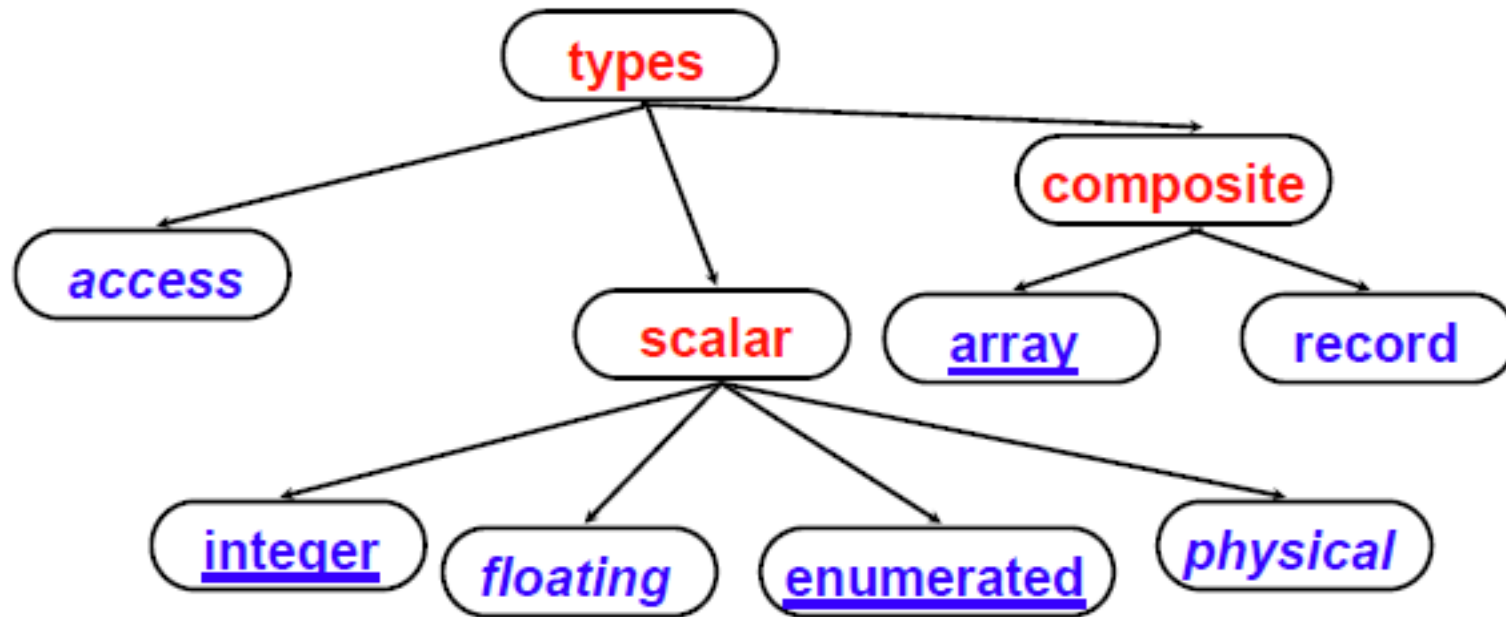All signals and variables must be declared of a defined type (or sub-type)



packages are design units (like entities and architecture) used to group definitions of data types and standard or commonly used operators (functions and procedures)

VHDL standard types

- definiti nel package **STANDARD** contenuto nella libreria **STD**
- presenti implicitamente in ogni simulatore VHDL

```
-- enumerazioni
TYPE boolean IS (false, true);
TYPE bit IS ('0', '1');
TYPE character IS (NUL, SOH,
    ..., 'a', 'b', 'c', ...);

-- interi
TYPE integer IS RANGE -2147483647
    TO + 2147483647;
SUBTYPE positive IS integer RANGE
    1 to integer'HIGH;
SUBTYPE natural IS integer RANGE
    0 to integer'HIGH;
```

```
-- reali
TYPE real IS RANGE -1E38 to 1E38;

-- fisici
TYPE time IS RANGE 0 TO NNN
    UNITS
        fs;
        ps = 1000 fs;
        ...
        hr = 60 min;
    END UNITS;

-- array
TYPE string IS ARRAY (POSITIVE
    RANGE <>) OF characters;
TYPE bit_vector IS ARRAY (NATURAL
    RANGE <>) OF bit;
```

VHDL data types: definition examples

```
TYPE byte_in IS RANGE 0 TO 255
TYPE s_word IS RANGE -32768 TO 32767
TYPE resistance IS RANGE 0 TO 1E8
  UNITS
    ohms;
    kohms = 1000 ohms;
    Mohms = 1000 kohms;
  END UNITS;
TYPE probability IS RANGE 0.0 TO 1.0
TYPE bit IS ('0', '1');
TYPE word IS ARRAY (0 TO 31) OF bit;
TYPE vector IS ARRAY (integer RANGE
  <>) OF real;
SUBTYPE bcd IS integer RANGE 0 TO 9;
```

} integer types

} physical types

} floating types

} enumeration types

} composite types

} subtypes

VHDL object types, arrays

- the index variation range of an array can be ascending or descending:
 - `SIGNAL a: bit_vector (3 downto 0);` -- discendente
 - `SIGNAL b: bit_vector (0 to 3);` -- ascendente
- array assignments are based on location:
 - `b <= a;` -- significa: `b(0) <= a(3); ...; b(3) <= a(0);`
 - `b(1 downto 0) <= a(3 downto 2);` -- assegnazione parziale, con inversione dell'ordine predefinito di `b`; il risultato è `b(1) <= a(3); b(0) <= a(2);`
 - `a <= ('1', '0', '1', '0');` -- assegnazione tramite aggregato
 - `a <= B"1010"` -- assegnazione tramite stringa di bit
 - `a <= X"A"` -- come sopra, ma in formato esadecimale
 - `a <= (OTHERS => '1');` -- assegnazione dello stesso valore a tutti gli elementi di `a`
 - `b & a` -- produce `(b(0), b(1), b(2), b(3), a(3), a(2), a(1), a(0))`

VHDL object types, arrays attributes

in the case of arrays, attributes provide additional information relative to the signal index

```
SIGNAL x: bit_vector(0 TO 3);  
SIGNAL y: bit_vector(3 DOWNTO 0);  
SIGNAL i: integer;  
  
-- attributi di valore:  
forniscono il valore minimo e  
massimo dell'indice, e il numero  
di elementi dell'array  
  
i <= x'LOW -- i = 0  
i <= y'LOW -- i = 0  
i <= x'HIGH -- i = 3  
i <= y'HIGH -- i = 3  
i <= x'LENGTH -- i = 4  
i <= y'LENGTH -- i = 4
```

```
-- attributi di posizione  
  
i <= x'LEFT; -- i = 0  
i <= y'LEFT; -- i = 3  
i <= x'RIGHT; -- i = 3  
i <= y'RIGHT; -- i = 0  
  
x'RANGE -- 0 TO 3  
y'RANGE -- 3 DOWNTO 0  
x'REVERSE_RANGE -- 3 DOWNTO 0  
y'REVERSE_RANGE -- 0 TO 3
```

VHDL standard operators and expressions

Operatori presenti nel package **STANDARD**:

- booleani: **not**, **and**, **nand**, **or**, **nor**, **xor**, **xnor**
- relazionali: **=**, **/=**, **<**, **<=**, **>**, **>=**
- shift: **sll**, **srl**, **sla**, **sra**, **rol**, **ror**
 - poco usati, hanno un comportamento non convenzionale
- aritmetici: **+**, **-**, **abs**, **+**, **-**, *****, **/**, **mod**, **rem**, ******
 - **segno** **operazioni**
- concatenazione: **&**
 - concatena due array, mettendo l'operando di destra in coda a quello di sinistra


VHDL tri-state logic

- La tipologia `bit` va molto bene per descrivere un hardware digitale ideale, in cui tutti i segnali hanno il valore logico '0' o '1'.
- Esistono situazioni nelle quali i due stati logici non sono più sufficienti.
- Un esempio di questa necessità si ha nella descrizione di una porta logica tri-state nella quale il segnale di uscita può assumere tre valori: '0', '1' e 'Z' (per indicare l'alta impedenza).
- Definiamo quindi un nuovo tipo:

```
type tri is ('0', '1', 'Z');
```


e quindi andare a definire porte e segnali:

```
signal a,b,c : tri;
```

 

VHDL tri-state logic

Oltre a definire la tipologia, però dobbiamo andare a definire tutte le varie funzioni in modo che abbiano ancora senso assegnazioni del tipo:

```
a <= '0' and '1' ;
```

```
b <= a or c;
```

Ad esempio la funzione **and** dovrà rispettare le regole dettate dalla tabella di verità qui a fianco

AND	0	1	Z
0	0	0	0
1	0	1	1
Z	0	1	1

Visto che questa esigenza è comune a tutti i progettisti la IEEE ha creato un pacchetto standard che permette di superare la limitazione della tipologia bit, fornendo anche tutte le relazioni fra i segnali.

VHDL Standard Logic Packet **STD_LOGIC_1164**

IEEE ha creato due package per tipi di dati (e relativi operatori) logici e aritmetici:

- **STD_LOGIC_1164**

- sistema a 9 stati logici

- **TYPE std_logic IS ('U' , 'X' , '0' , '1' , 'Z' , 'W' , 'L' , 'H' , '-') ;**

- "U" Non definito (a cui non è mai stato dato un valore)

- "X" Sconosciuto (il cui valore non è determinabile)

- "0" 0 logico

- "1" 1 logico

- "Z" Alta impedenza

- "W" Segnale debole, senza un valore determinabile

- "L" Segnale debole che probabilmente andrà a 0

- "H" Segnale debole che probabilmente andrà a 1

- "-" Indifferente (*Don't care*)

- **TYPE std_logic_vector IS ARRAY (NATURAL RANGE <>) OF std_logic;**

VHDL Arithmetic Logic Packets

Oltre al pacchetto **STD_LOGIC_1164** con tutte le funzioni logiche si è visto che è utile andare a definire anche tutte le funzioni aritmetiche su questo tipo di dati; per questo la IEEE ha creato due diversi pacchetti (che possono essere utilizzati in alternativa).

- **NUMERIC_STD**

- **TYPE unsigned IS ARRAY (NATURAL RANGE <>) OF std_logic;**
- **TYPE signed IS ARRAY (NATURAL RANGE <>) OF std_logic;**
- **unsigned** interpretato come rappresentazione binaria di un intero senza segno;
- **signed** interpretato come rappresentazione in complemento a 2 di un intero

- **STD_LOGIC_ARITH**

- alternativa (preferita) a **NUMERIC_STD**

VHDL Packet: STD_LOGIC_(UN) SIGNED

- la libreria IEEE contiene anche i due package **STD_LOGIC_UNSIGNED** e **STD_LOGIC_SIGNED**
- sono in alternativa l'uno all'altro e introducono operatori e funzioni che interpretano i dati di tipo **STD_LOGIC_VECTOR** come numeri binari rispettivamente senza e con segno:

```
function "+"(L: STD_LOGIC_VECTOR; R: STD_LOGIC_VECTOR)
    return STD_LOGIC_VECTOR;
function "+"(L: STD_LOGIC_VECTOR; R: INTEGER) return
    STD_LOGIC_VECTOR;
...
function CONV_INTEGER(ARG: STD_LOGIC_VECTOR) return
    INTEGER;
```

VHDL Libraries

- [illegible]

VHDL Concurrent Instructions

Concurrent instructions

- used within the architecture to describe the signal behavior
- activated (or executed) only after an event on one of the signals to which they are sensitive
- the order of execution does not depend from the order with which they appear in the model
 - **“parallel” signal processing**

- inside a process

```
--with sensitivity list
P1: PROCESS (a,b)
BEGIN
  z <= a NOR b;
END PROCESS;
--with wait instruction
P2: PROCESS
BEGIN
  z <= a NOR b;
  WAIT ON a, b;
END PROCESS;
```

- conditional assignments

```
-- not in a process
ARCHITECTURE rtl OF ...
BEGIN
  -- simplest
  z <= a NOR b;
  -- priority conditional assignment
  a <= b WHEN sel=B"00" ELSE c WHEN
    sel=B"01" ELSE d;
  a <= b WHEN sel=B"00" ELSE c WHEN
    sel=B"01" ELSE UNAFFECTED;
  -- conditional without priority
  WITH sel SELECT
    a <= b WHEN B"00",
    c WHEN B"01",
    d WHEN OTHERS;
```

VHDL Sequential Instructions

Sequential instructions

- they are user only inside a process,
- they are executed following the order with which they appear in the model
→ “serial” signal processing

- wait

```
WAIT ON x UNTIL y=0 FOR 12 NS;
```

- esecuzioni condizionate

```
-- choices with priority
```

```
IF sel = B"00" THEN
```

```
    z_out := a;
```

```
ELSIF sel = B"01" THEN
```

```
    z_out := b;
```

```
ELSE
```

```
    z_out := c;
```

```
ENDIF
```

```
-- choices without priority
```

```
CASE sel IS
```

```
    WHEN B"00" => z_out := a;
```

```
    WHEN B"01" => z_out := b;
```

```
    WHEN OTHERS => z_out := c;
```

```
END CASE;
```

- loop

```
WHILE i < nmax LOOP
```

```
    z(i) := x(i);
```

```
    i := i + 1;
```

```
END LOOP;
```

```
FOR k IN 1 TO n LOOP
```

```
    table(k) := 0;
```

```
END LOOP
```

- NEXT, EXIT, NULL

```
NEXT; -- interrompe l'iterazione
```

```
-- corrente in un loop e passa
```

```
-- alla successiva
```

```
EXIT; -- interrompe il loop
```

```
NULL; -- non fa niente; utile
```

```
-- nei CASE e IF se si desidera
```

```
-- che a certe scelte non
```


```
--corrisponda alcuna azione
```

VHDL Variables vs Signals


→ sequential/
concurrent

variables: sequential alternative for signal processing
 
```
ARCHITECTURE test1 OF mux IS
  SIGNAL a,x,y : BIT := '0';
BEGIN
  PROCESS (a)
  BEGIN
    x <= a;
    y <= x;
  END PROCESS;
END test1;
```


 
```
ARCHITECTURE test2 OF mux IS
  SIGNAL a,y : BIT := '0';
BEGIN
  PROCESS (a)
    VARIABLE x : BIT := '0';
  BEGIN
    x := a;
    y <= x;
  END PROCESS;
END test2;
```



The **process** is executed when **a** value changes (from 0 to 1, in the example above);

- In the first case, **x** takes the value of **a** at the end of the process, whereby **y** is assigned to the original value of **x** (i.e. 0) (concurrent/parallel execution)

- In the second case, **x** takes the value of **a** when the assignment **x := a** is executed (sequential/serial execution) then **y** assumes the new value of **x**

VHDL Procedures and Functions

- dichiarazione

```
PROCEDURE p_and(CONSTANT a, b: IN bit; classeSIGNAL direzionec: tipoOUT bit);
```

- direzione IN, OUT, INOUT; classe CONSTANT, VARIABLE, SIGNAL

- non ritorna parametri

```
FUNCTION f_and(CONSTANT a, b: IN bit) RETURN bit;
```

- solo direzione IN (non può modificare i parametri)

- definizione (*body*)

```
PROCEDURE p_and(CONSTANT a, b: IN bit; SIGNAL c: OUT bit) IS
```

```
    BEGIN    c <= a AND b; END;
```

```
FUNCTION f_and(CONSTANT a, b: IN bit) RETURN bit IS
```

```
    BEGIN    RETURN a AND b; END
```

- chiamata

```
p_and(x1, x2, y); -- scrive direttamente il risultato in y
```

```
y <= f_and(x1, x2); -- ritorna il risultato che poi viene assegnato a y  
                    esternamente alla funzione
```

III – Architecture structure and Concurrent / Sequential execution

An architecture definition has two parts: declarative and statement

- declarative part: objects internal to the architecture may be defined
- statement part: contains **concurrent statements** which define the **processes** or **interconnected blocks** that describe the operation or the **global structure of the system**

All **processes** in an architecture are executed **concurrently** with each other, but the **statements** within a process are executed **sequentially**

A suspended process is activated again when one of the signals in its **sensitivity list** changes its value. When there are multiple processes in an architecture, if a signal changes its value then all processes that contain this signal in their sensitivity lists are activated. The **statements within the activated processes are executed sequentially, but independently** from the statements in other processes

Communication among **processes** is achieved using **concurrent signal assignment** statements

Concurrent and Sequential

Sequential statements are executed in the order in which they appear within the process or subprogram
(as in programming languages)

Concurrent statements are executed in parallel
(the operations in real systems are executed concurrently)

Signals represent the **interface** between the two domains:

- the Concurrent domain VHDL model and
- the Sequential domain within processes

Sequential statements

Sequential statements:

- **Processes** are composed of sequential statements ...
... but process declarations are concurrent statements
- **Sequential Signal assignment**
- **Variable assignment**
- **if** statement, **case** statement, **loop** statements
(loop, while loop, for loop, next, exit)
- sequential **assert** statement
- **procedure** call statement
- **return** statement from a procedure or function

Processes

Sequential statements

```
[name:] process [(sensitivity_list)]  
    [type_declarations]  
    [constant_declarations]  
    [variable_declarations]  
    [subprogram_declarations]  
begin  
    sequential_statements  
end process [name];
```

Note:
no Signal declaration
allowed in a process

When the **sensitivity list is missing**, the process will be run continuously

In this case, the process must contain a **wait** statement to suspend the process and to activate it when an event occurs or a condition becomes true

When the sensitivity list is present, the process cannot contain **wait** statements

Processes

Sequential statements

```
proc1: process (a, b, c)
begin
    x <= a and b and c;
end process proc1;

proc2: process (a, b)
begin
    x <= a and b and c;
end process proc2;
```

```
proc3: process
begin
    x <= a and b and c;
    wait on a, b, c;
end process proc3;
```

Wait Statement Forms

There are three forms of the wait statement:

```
wait on sensitivity_list;
wait until conditional_expression;
wait for time_expression;
```

When the **sensitivity list is missing**, the process will be run continuously

In this case, the process must contain a **wait** statement to suspend the process and to activate it when an event occurs or a condition becomes true

When the sensitivity list is present, the process cannot contain wait statements

Wait statement examples

```
wait until signal = value;  
wait until signal'event and signal = value;  
wait until not signal'stable and signal = value;
```

Synchronous operations

```
wait until clk = '1';  
wait until clk'event and clk = '1';  
wait until not clk'stable and clk = '1';
```


Processes

Combinatorial vs Sequential

Both combinational and sequential processes are interpreted in the same way, the only difference being that for **sequential processes the output signals are stored into registers**


combinational
 
```
proc5: process
begin
    wait on a, b;
    z <= a and b;
end process proc5;
```



sequential
 
```
proc6: process
begin
    wait until clk = '1';
    z <= a and b;
end process proc6;
```



Note: **please always consider the hardware behind what you write !**

Seq. Signal Assignment

- Signals** represent the interface between
- the Concurrent domain VHDL model and
 - the Sequential domain within processes

Signal assignment may be performed using a **sequential** statement or a **concurrent** statement:

- The **sequential** statement may only appear **inside a process**
- The **concurrent** statement may only appear **outside processes**

The **sequential** signal assignment has

- a single form (the **simple** one i.e. unconditional assignment)

The **concurrent** signal assignment has

- in addition to its **simple** form, two other forms:
- the **conditional** assignment and
- the **selective** assignment

Note: see examples of simple forms in previous slide

Seq. Signal Assignment

```
signal <= expression
```

As a result of executing this statement in a process, the expression on the right-hand side of the assignment symbol is evaluated and an event is scheduled to change the value of the signal (see simulator example)

The simulator will only **change the value of a signal when the process suspends**. Therefore, in a process the **signals will be updated only after executing all the statements** of the process or when a wait statement is encountered

Consequence #1: only **last assignment** to same signal will be executed

```
proc7: process (a)
begin
    z <= '0';
    z <= a;
end process proc7;
```



```
proc8: process (a)
begin
    z <= a;
end process proc8;
```


Seq. Signal Assignment

signal <= expression


As a result of executing this statement in a process, the expression on the right-hand side of the assignment symbol is evaluated and an event is scheduled to change the value of the signal (see simulator example)

The simulator will only **change the value of a signal when the process suspends**. Therefore, in a process the **signals will be updated only after executing all the statements** of the process or when a wait statement is encountered

Consequence #2: feedback !!! (new assignment depending on signal history)

```
library ieee;
use ieee.numeric_bit.all;

 signal count: unsigned (3 downto 0);
process
begin
    wait until clk = '1';
    if reset = '1' then
        count <= "0000";
    else
        count <= count + "0001";
    end if;
end process;
```



Seq. Signal Assignment

Another consequence of the way in which signal assignments are executed is that any reading of a signal that is also assigned to in the same process will return the value assigned to the signal in the previous execution of the process (reading a **signal and assigning a value to it** in the **same process** is equivalent to a *feedback*)


In a **combinational process**, the previous value is an output of the combinational logic and so the **feedback is asynchronous**

In a **sequential process**, the previous value is the value stored in a latch or register, so the **feedback is synchronous**.

Consequence #2: feedback !!!

```
library ieee;
use ieee.numeric_bit.all;

 signal count: unsigned (3 downto 0);
process
begin
    wait until clk = '1';
    if reset = '1' then
        count <= "0000";
    else
        count <= count + "0001";
    end if;
end process;
```



Variable Assignment

Sequential statements

Signal drawbacks:

- can only **hold the last value assigned to them** → they cannot be used to store intermediary results within a process
- **new values** are not assigned to signals when the assignment statement executes, but **only after the process execution suspends**

Variables:

- can be declared inside (and only inside) processes: **local to processes** (only in sequential domain, not in architectures)
- can **store intermediate results** → **many assignment are possible**
- are **updated immediately** (immediate execution of assignment)

Assigned

variable := expression;

Declared

```
variable a, b, c: bit;  
variable x, y: integer;  
variable index range 1 to 10 := 1;  
variable cycle_t: time range 10 ns to 50 ns := 10 ns;  
variable mem: bit_vector (0 to 15);
```

Variable Assignment

Sequential statements

```
entity add_1 is
  port (a, b, cin: in bit;
        s, cout: out bit);
end add_1;

architecture functional of add_1 is
begin
  process (a, b, cin)
    variable s1, s2, c1, c2: bit;
  begin
    s1 := a xor b;
    c1 := a and b;
    s2 := s1 xor cin;
    c2 := s1 and cin;
    s <= s2;
    cout <= c1 or c2;
  end process;
end functional;
```

full-adder made of two
half-adders
(not the optimal way...)

If statement


```
if condition then statement_sequence
  [elsif condition then statement_sequence...]
  [else statement_sequence]
end if;
```

Conditions are Boolean expressions (TRUE / FALSE)

If statemets synthesised as **Multiplexer**

```
library ieee;
use ieee.numeric_bit.all;
entity comp is
  port (a, b: in unsigned (7 downto 0);
        equal: out bit);
end comp;

 architecture functional of comp is
begin
  process (a, b)
  begin
    if a = b then
      equal <= '1';
    else
      equal <= '0';
    end if;
  end process;
end functional;
```



If statement

Warning:

must always describe every possible condition !


Incomplete If statemets result in **feedback**

(ie signal new assignment depending on signal hystory, not on present values)

```
process
begin
    wait until clk = '1';
    if en = '1' then
        q <= d;
    end if;
end process;
```

implicit : else

```
    q <= q;
end if;
```

 

feedback !

If statement

Variables can be used in IF statements, allowing uses of feedback

```
process
  variable count: unsigned (7 downto 0);
begin
  wait until clk = '1';
  if reset = '1' then
    count := "00000000";
  else
    count := count + 1;
  end if;
  result <= count;
end process;
```

Case statement

Case statement is like If statement but:

- allows selection based on expression (not just boolean)
- all choices depend on the same input and are mutually exclusive

```
case expression is  
  when options_1 =>  
    statement_sequence  
  ...  
  when options_n =>  
    statement_sequence  
  [when others =>  
    statement_sequence]  
end case;
```

Case statements synthesised as [Multiplexer](#)

Loop statements

Loop statements allow repeated execution of a statement sequence

→ eg processing each element of an array

```
[label:] for counter in range loop  
    statement_sequence  
end loop [label];
```

```
for i in 1 to 10 loop  
    i_square (i) <= i * i;  
end loop;
```

```
for i in integer range 1 to 10 loop
```

Loop statements

Sequential statements

```
entity match_bits is
    port (a, b: in bit_vector (7 downto 0);
          matches: out bit_vector (7 downto 0));
end match_bits;

architecture functional of match_bits is
begin
    process (a, b)
    begin
        for i in 7 downto 0 loop
            matches (i) <= not (a(i) xor b(i));
        end loop;
    end process;
end functional;
```

This loop is synthesised as
a set of 1-bit comparators
to compare bits of the same
order of vectors a and b
→ equivalent to:

```
process (a, b)
begin
    matches (7) <= not (a(7) xor b(7));
    matches (6) <= not (a(6) xor b(6));
    matches (5) <= not (a(5) xor b(5));
    matches (4) <= not (a(4) xor b(4));
    matches (3) <= not (a(3) xor b(3));
    matches (2) <= not (a(2) xor b(2));
    matches (1) <= not (a(1) xor b(1));
    matches (0) <= not (a(0) xor b(0));
end process;
```

(order of the executions
not relevant ...
... concurrent execution)

Loop statements

Sequential statements


```
library ieee;
use ieee.numeric_bit.all;
entity count_ones is
    port (v: in bit_vector (15 downto 0);
          count: out signed (3 downto 0));
end count_ones;

architecture functional of count_ones is
begin
    process (v)
        variable result: signed (3 downto 0);
    begin
        result := (others => '0');
        for i in 15 downto 0 loop
            if v(i) = '1' then
                result := result + 1;
            end if;
        end loop;
        count <= result;
    end process;
end functional;
```

This is a combinational circuit which counts the number of bits in vector v that are set to '1'

The result is accumulated during the execution of the process in a variable called result and then assigned to the output signal count at the end of the process

 The loop body – if statement containing a variable assignment – represents a block containing a multiplexer and an adder, which will be generated by synthesis for each iteration of the loop. The output of a block becomes the input result of the next block...



If statement

Variables can be used in IF statements

If a variable is assigned to only in some branches of the IF statement then
→ previous value is preserved by **feedback** !!! Unlike the case when a signal is used, the reading and writing of a variable in the same process will result in feedback **only if the read occurs before the write**

In this case, the value read is the previous value of the variable

→ this may be used to **create registers or counters using variables**

Remember that a **sequential process is interpreted by synthesis by placing a flip-flop** (or register, ie flip-flop array) on every signal assigned to in the process, then

→ **normally variables are not written to flip-flops or registers unless there is feedback of a previous variable value**, then

→ this feedback is implemented via a flip-flop or register to make the process synchronous

Concurrent statements

Concurrent statements:

- **Process** declarations are concurrent statements
- **Concurrent Signal assignment**
- **Block statements**
- concurrent **assert** statement
- concurrent **procedure** call statement
- **component** instantiation statement
- **generate** statement

Architecture structure

and execution

An architecture definition has two parts: declarative and statement

- declarative part: objects internal to the architecture may be defined
- statement part: contains **concurrent statements** which define the **processes** or **interconnected blocks** that describe the operation or the **global structure of the system**

All **processes** in an architecture are executed **concurrently** with each other, but the **statements** within a process are executed **sequentially**

A suspended process is activated again when one of the signals in its sensitivity list changes its value. When there are multiple processes in an architecture, if a signal changes its value then all processes that contain this signal in their sensitivity lists are activated. The **statements within the activated processes are executed sequentially, but independently** from the statements in other processes

Communication among processes is achieved using **concurrent signal assignment** statements

(can be used eg for synchronization). Note: variables cannot be used

Architecture structure

and execution

```
entity add_1 is
  port (a, b, cin: in bit;
        s, cout: out bit);
end add_1;

architecture processes of add_1 is
  signal s1, s2, s3, s4: bit;
begin

  p1: process (b, cin)
  begin
    s1 <= b xor cin;
  end process p1;

  p2: process (a, b)
  begin
    s2 <= a and b;
  end process p2;

  p3: process (a, cin)
  begin
    s3 <= a and cin;
  end process p3;


  p4: process (b, cin)
  begin
    s4 <= b and cin;
  end process p4;

  p5: process (a, s1)
  begin
    s <= a xor s1;
  end process p5;

  p6: process (s2, s3, s4)
  begin
    cout <= s2 or s3 or s4;
  end process p6;

end processes;
```

full-adder

 

Process (summary)

- It is executed in **parallel** with other processes;
- It **cannot contain concurrent** statements;
- It defines a region of the architecture where statements are executed **sequentially**;
- It must contain an **explicit sensitivity list** or **a wait statement**;
- It allows **functional descriptions**, similar to the programming languages;
- It allows access to signals defined in the architecture in which the process appears and to those defined in the entity to which the architecture is associated.

Concurrent signal assignment

→ simple version

Concurrent statements

This statement is the **concurrent version of the sequential** signal assignment statement and has the **same form with this**

As the sequential version, the concurrent assignment **defines a new driver for the assigned signal**

A **concurrent assignment statement** appears outside a process, within an architecture. A concurrent assignment statement represents a **simplified form of writing a process**

→ it is **equivalent to a process that contains a single sequential assignment statement**


Concurrent signal assign. → simple version

Concurrent statements

```
entity add_1 is
    port (a, b, cin: in bit;
          s, cout: out bit);
end add_1;

architecture concurrent of add_1 is
    signal s1, s2, s3, s4: bit;
begin
    s1 <= b xor cin;
    s2 <= a and b;
    s3 <= a and cin;
    s4 <= b and cin;
    s  <= a xor s1;
    cout <= s2 or s3 or s4;
end concurrent;
```

!!! full-adder

 

Nota: the order in which the statements are written is not relevant

Concurrent signal assign.

Concurrent statements

→ conditional version

The conditional assignment statement is functionally equivalent to the `if` conditional statement:

```
signal <= [expression when condition else ...]  
           expression;
```

The differences are:

- the conditional assignment statement is a concurrent statement and therefore it can be used in an architecture, while the `if` statement is a sequential statement and can be used only inside a process
- the conditional assignment statement can only be used to assign values to signals, while the `if` statement can be used to execute any sequential statement

Note: the hardware behind is different:

- all possible drivers for the same signal are prepared
- though they are evaluated with some order

Concurrent signal assign. → conditional version

```
entity xor2 is
  port (a, b: in bit;
        x: out bit);
end xor2;
```


```
architecture arch1_xor2 of xor2 is
begin
  x <= '0' when a = b else
    '1';
end arch1_xor2;
```

concurrent conditional assignment

```
architecture arch2_xor2 of xor2 is
begin
  process (a, b)
  begin
    if a = b then x <= '0';
    else x <= '1';

    end if;
  end process;
end arch2_xor2;
```

sequential conditional statement

 


implemented as Multiplexer

Concurrent signal assign.


Concurrent statements

→ conditional version – additional examples
 
```
s <= a xor b when c = '1' else  
    not (a xor b);
```


 
```
z <= a when s0 = '1' else  
    b when s1 = '1' else  
    c;
```



Concurrent signal assign.

→ selected version

```
with selection_expression select  
    signal <= expression_1 when options_1,  
        ...  
    expression_n when options_n,  
    [expression when others];
```

Like the conditional signal assignment statement, the selected signal assignment statement allows to select a source expressions based on a condition

The difference is that the selected signal assignment statement uses a **single condition** to select between **several options**

This statement is functionally **equivalent to the case sequential statement**

A `block` statement defines a group of concurrent statements.

This statement is useful to hierarchically organize the concurrent statements or to partition a list of structural interconnections in order to improve readability of the description

```
label: block [(guard_expression)]  
    [declarations]  
begin  
    concurrent_statements  
end block [label];
```

The mandatory label identifies the block

In the declaration part, local objects of the block may be declared

The possible declarations are those that may appear in the declarative part of an architecture

- Use clauses;
- Port and generic declarations, as well as port map and generic map declarations;
- Subprogram declarations and bodies;
- Type and subtype declarations;
- Constant, variable, and signal declarations;
- Component declarations;
- File, attribute, and configuration declarations.

The order of concurrent statements is not relevant ...

IV - VHDL examples


- Multiplexers
- Adders
- Memory elements: latch and flip-flop
- Registers

Reminder

- Asynchronous sequential circuits: Latches
- Synchronous circuits: Flip-Flops, Counters, Registers
- Synthesis inference rules

VHDL examples: MULTIPLEXER 4→1

 esempio con istruzione concorrente WITH SELECT



```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
USE IEEE.STD_LOGIC_ARITH.ALL;

ENTITY mux4to1 IS
    PORT(x: IN std_logic_vector(3
        DOWNTO 0);
        s: IN unsigned(1 DOWNTO 0);
        z: OUT std_logic);
END mux4to1;

ARCHITECTURE bhv1 OF mux4to1 IS
BEGIN
    WITH s SELECT
        z <= x(0) WHEN "00",
        z <= x(1) WHEN "01",
        z <= x(2) WHEN "10",
        z <= x(3) WHEN OTHERS;
END bhv1;
```

VHDL examples: MULTIPLEXER 4→1

esempio con istruzione sequenziale CASE all'interno di un processo


```
ARCHITECTURE bhv2 OF mux4to1 IS
BEGIN
  -- il processo è concorrente: viene
  -- eseguito solo in seguito a eventi
  -- su s o x
  PROCESS (s,x) BEGIN
    -- le istruzioni contenute nel
    -- processo vengono eseguite in
    -- sequenza; in questo esempio c'è
    -- una sola istruzione (CASE ...
    -- END CASE;)
    CASE s IS
      WHEN "00" => z <= x(0);
      WHEN "01" => z <= x(1);
      WHEN "10" => z <= x(2);
      WHEN OTHERS => z <= x(3);
    END CASE;
  END PROCESS;
END bhv2;
```

VHDL examples: MULTIPLEXER 4→1

 esempio con istruzione sequenziale
IF ... THEN ... ELSE

```
ARCHITECTURE bhv4 OF mux4to1 IS
BEGIN
  PROCESS (s, x)
  BEGIN
    IF s = "00" THEN
      z <= x(0);
    ELSIF s = "01" THEN
      z <= x(1);
    ELSIF s = "10" THEN
      z <= x(2);
    ELSE
      z <= x(3);
    END IF;
  END PROCESS;
END bhv4;
```

è un uso improprio di **IF ... THEN ... ELSE** perché questa istruzione, in fase di sintesi, ha una interpretazione gerarchica:



VHDL examples: ADDER (behav. architecture)


esempio di architettura di tipo comportamentale (*behavioral*): descrive solo la sequenza di operazioni necessarie a ottenere le uscite dagli ingressi

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
USE ieee.std_logic_arith.all;
```

```
ENTITY adder IS  
  GENERIC (N: integer := 16);  
  PORT (ci : IN  std_logic;  
        x,y: IN  signed(N-1 DOWNTO 0);  
        s  : OUT signed(N-1 DOWNTO 0);  
        co : OUT std_logic);  
END adder;
```

```
ARCHITECTURE bhv OF adder IS  
  SIGNAL sum: signed(N DOWNTO 0);  
BEGIN  
  sum <= ('0' & x) + y + ci;  
  s    <= sum(N-1 DOWNTO 0);  
  co   <= sum(N);  
END bhv;
```

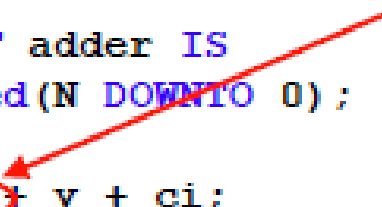concatenazione: porta
il numero di bit a 17,
come sum



VHDL examples: ADDER (ripple-carry)

il processo con il ciclo **FOR** crea una architettura di tipo ripple-carry

```
ARCHITECTURE rtl OF adder IS                                ! sequential version
BEGIN                                                         (inside a process)
    PROCESS (x,y,ci)
        -- l'array carry è una variable quindi il suo valore viene aggiornato nel
        -- momento stesso in cui viene eseguita l'assegnazione carry(i) := ...
        VARIABLE carry: std_logic_vector(N-1 DOWNT0 0);
    BEGIN
        FOR i IN x'REVERSE_RANGE LOOP
            IF i=0 THEN
                carry(i) := (x(i) AND y(i)) OR (x(i) AND ci) OR (y(i) AND ci);
                s(i) <= x(i) XOR y(i) XOR ci;
            ELSE
                carry(i) := (x(i) AND y(i)) OR (x(i) AND carry(i-1)) OR
                           (y(i) AND carry(i-1));
                s(i) <= x(i) XOR y(i) XOR carry(i-1);
            END IF;
        END LOOP;
        co <= carry(N-1);
    END PROCESS;
END rtl;
```

VHDL examples: ADDER (ripple-carry)

generate è un'istruzione concorrente usata per creare repliche di istruzioni concorrenti (quindi anche di processi); può creare un numero fissato di repliche (**FOR** ... **GENERATE**) oppure può sottostare ad una condizione (**IF** ... **GENERATE**)

```
ARCHITECTURE rtl2 OF adder IS
    SIGNAL carry: std_logic_vector(N-1 downto 0);
BEGIN
    G1: FOR i IN x' RANGE GENERATE
        G2: IF i = 0 GENERATE
            carry(i) <= (x(i) AND y(i)) OR (x(i) AND ci) OR (y(i) AND ci);
            s(i)      <= x(i) XOR y(i) XOR ci;
        END GENERATE;
        G3: IF i > 0 GENERATE
            carry(i) <= (x(i) AND y(i)) OR (x(i) AND carry(i-1)) OR
                        (y(i) AND carry(i-1));
            s(i)      <= x(i) XOR y(i) XOR carry(i-1);
        END GENERATE;
    END GENERATE;
    co <= carry(N-1);
END rtl2;
```

! concurrent version
(no process)

VHDL examples: ADDER (ripple-carry)

generate viene anche usato all'interno di descrizioni strutturali per creare una sequenza di istanze dello stesso componente; supponiamo ad esempio di voler realizzare un MUX 16-1 usando 5 MUX 4-1 come quello visto prima:

<pre>LIBRARY ieee; USE ieee.std_logic_1164.all; USE ieee.std_logic_arith.all; ENTITY mux16to1 IS PORT(x: IN std_logic_vector(15 DOWNT0 0); s: IN unsigned(3 DOWNT0 0); z: OUT std_logic); END mux16to1; ARCHITECTURE str OF mux16to1 IS SIGNAL m: std_logic_vector(3 DOWNT0 0);</pre>	<pre>-- dichiaro il componente che uso -- nella netlist COMPONENT mux4to1 PORT(x: IN std_logic_vector(3 DOWNT0 0); s: IN unsigned(1 DOWNT0 0); z: OUT std_logic); BEGIN G1: FOR i IN 0 TO 3 GENERATE level1: mux4to1 PORT MAP(x(4*i+3),x(4*i+2),x(4*i+1), x(4*i),s(1 DOWNT0 0),m(i)); END GENERATE; level2: mux4to1 PORT MAP(m(3),m(2),m(1),m(0), s(3 DOWNT0 2),z); END str;</pre>
---	---

! concurrent version
(no process)

VHDL examples: Latch and Flip-Flop

ci sono diversi modi per descrivere il funzionamento di un latch e di un flip-flop in VHDL; tuttavia, solo rispettando certe regole, il codice viene riconosciuto in modo corretto in fase di sintesi

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY latch IS
    PORT(d,clk: IN  std_logic;
         q      : OUT std_logic);
END latch;


ARCHITECTURE bhv OF latch IS
BEGIN
    PROCESS(d,clk)
    BEGIN
        IF clk = '1' THEN
            q <= d;
        END IF;
    END PROCESS;
END bhv;
```

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY dff IS
    PORT(d,clk: IN  std_logic;
         q      : OUT std_logic);
END dff;


ARCHITECTURE bhv OF dff IS
BEGIN
    PROCESS(clk)
    BEGIN
        IF clk'EVENT AND clk='1' THEN
            q <= d;
        END IF;
    END PROCESS;
END bhv;
```


VHDL examples: flip-flop w/ asynchronous and synchronous reset



```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY dffr IS
  PORT(d,clk,res: IN  std_logic;
        q: OUT std_logic);
END dffr;
ARCHITECTURE bhv OF dffr IS
BEGIN
  PROCESS(res,clk)
  BEGIN
    IF res = '1' THEN
      q <= '0';
    ELSIF clk'EVENT AND clk='1' THEN
      q <= d;
    END IF;
  END PROCESS;
END bhv;
```



```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY dffr IS
  PORT(d,clk,res: IN  std_logic;
        q: OUT std_logic);
END dffr;
ARCHITECTURE bhv2 OF dffr IS
BEGIN
  PROCESS BEGIN
    WAIT UNTIL clk'EVENT AND clk='1';
    IF res = '1' THEN
      q <= '0';
    ELSE
      q <= d;
    END IF;
  END PROCESS;
END bhv2;
```

VHDL examples: n-bit register

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY regn IS
  GENERIC(n: INTEGER := 16);
  PORT(d: IN std_logic_vector(n-1 DOWNT0 0);
       res,clk: IN std_logic;
       q: OUT std_logic_vector(n-1 DOWNT0 0));
END regn;
ARCHITECTURE bhv OF regn IS
BEGIN
  PROCESS(res,clk)
  BEGIN
    IF res = '1' THEN
      q <= (OTHERS => '0');
    ELSEIF clk'EVENT AND clk='1' THEN
      q <= d;
    END IF;
  END PROCESS;
END bhv;
```

valore di default; può essere
cambiato con **generic map**
quando il registro viene istanziato

non sapendo quanti bit ha **q**,
usiamo **others** per assegnare a
tutti il valore '0'

VHDL examples: shift register

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
ENTITY shift IS
    GENERIC(n: INTEGER := 16);
    PORT(r: IN std_logic_vector(n-1 DOWNT0 0);
         load,clk,w: IN std_logic;
         q: OUT std_logic_vector(n-1 DOWNT0 0));
END shift;
ARCHITECTURE bhv OF shift IS
    SIGNAL qi: std_logic_vector(n-1 DOWNT0 0);
BEGIN
    PROCESS(clk)
    BEGIN
        IF clk'EVENT AND clk='1' THEN
            IF load = '1' THEN
                qi <= r;
            ELSE
```

qi(i) viene aggiornato al termine
del processo, quindi per tutto il
ciclo FOR i segnali qi(i)
conservano il valore iniziale

```
                qi(qi'RIGHT) <= w;
                FOR i IN 1 TO qi'LEFT LOOP
                    qi(i) <= qi(i-1);
                END LOOP;
            END IF;
        END IF;
    END PROCESS;
    q <= qi;
END bhv;
```

V - Finite State Machines

A system that

- jumps from one state to the next
- within a pool of finite states
- upon clock edges and input transitions


Examples: traffic light, digital watch, CPU, ...

Reminder: Combinatorial vs Sequential circuits

Both combinational and sequential processes are interpreted in the same way, the only difference being that for **sequential processes** the output signals are stored into registers


Combinatorial
 
```
proc5: process
begin
    wait on a, b;
    z <= a and b;
end process proc5;
```



Sequential

 
```
proc6: process
begin
    wait until clk = '1';
    z <= a and b;
end process proc6;
```




Reminder: Combinatorial vs Sequential

- In combinational circuits, the output only depends upon the present input values.
- There exist another class of logic circuits whose outputs not only depend on the present input values but also on the past values of inputs, outputs, and/or internal signal. These circuits include storage elements to store those previous values.
- The content of those storage elements represents the *circuit state*. When the circuit inputs change, it can be that the circuit stays in certain state or changes to a different one. Over time, the circuit goes through a sequence of states as a result of a change in the inputs. The circuits with this behavior are called *sequential circuits*.


COMBINATIONAL CIRCUIT

 

SEQUENTIAL CIRCUIT

 

General Sequential Systems

 


General Sequential systems are such that past input values either are

- either **stored explicitly** or
- **cause the system to enter** a particular state

→ working principles are **feed-forward** and **feed-back**

General Sequential Systems

 


Sequential
synchronous

The present state of the system can be updated

- either as soon as the **next state changes** → asynchronous
- or only when a **clock signal changes** → synchronous

Synchronous systems are simpler → start with them

Finite State Machine

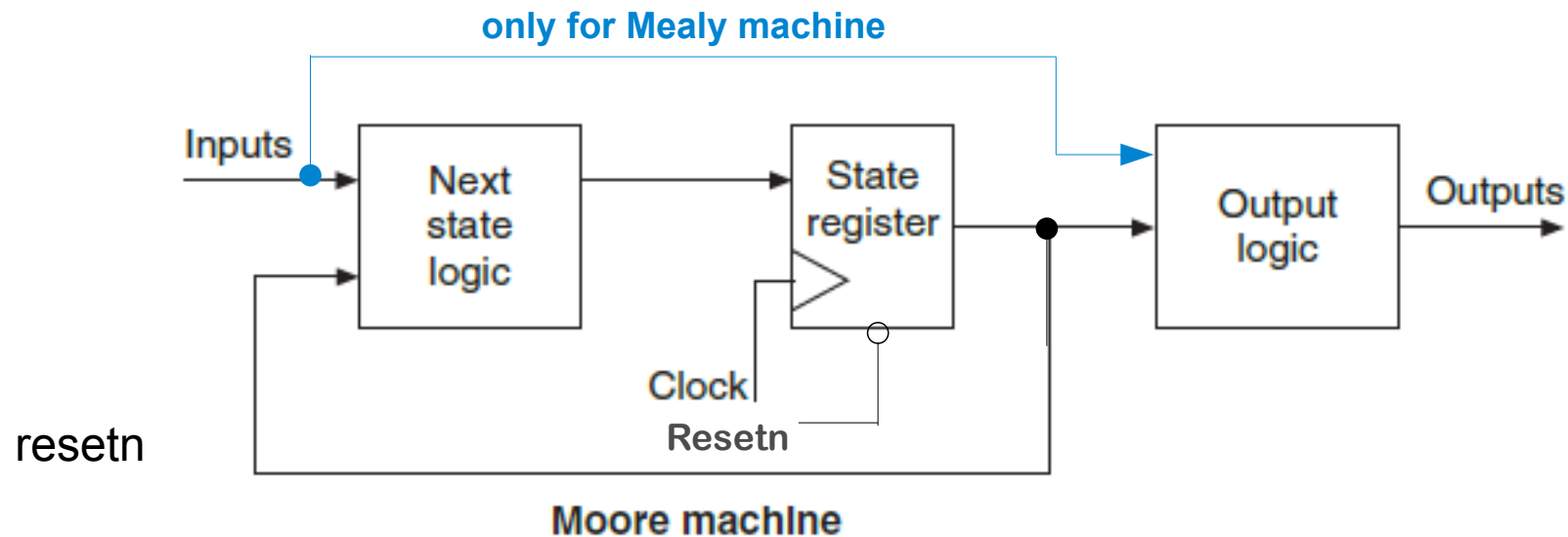

Two common models of synchronous sequential systems

- **Moore Machine:** Outputs depend only on the current state of the circuit
- **Mealy Machine:** Outputs depend on the current state of the circuit as well as the inputs of the circuit

Note: the circuit must always start from an initial state



→ there should be a 'resetrn' signal

About FSM registers

Combinational logic can contain hazards ! The next state logic of the Moore and Mealy machines is simply a block of combinational logic with a number of inputs and a number of outputs. The existence of hazards in the next state logic could cause the system to go to an incorrect state. There are two ways to avoid that:

  - 1) either the next state logic should include the redundant logic needed to suppress the hazard
- 2) the state machine should be designed such that a hazard is allowed to occur, but is ignored ← **this approach is usually adopted**

To ensure that sequential systems are able to ignore hazards,
→ **a clock is used to synchronize data**





D	C	Q^+	\bar{Q}^+
0	↑	0	1
1	↑	1	0
-	0	Q	\bar{Q}
-	1	Q	\bar{Q}

About edge triggered FF


Flip Flops:

  - The edge detector circuit generates $E=1$ during the edge (rising or falling). We will work with circuits activated by either rising or falling edge. We will not work with circuits activated by both edges.
- An example of a circuit that detects a rising edge is shown below. The redundant NOT gates cause a delay that allows a pulse to be generated during a rising edge (or positive edge).



About edge triggered FF

▪ D Flip Flop

 


clock	D	Q_{t+1}
	0	0
	1	1


```
library ieee;  
use ieee.std_logic_1164.all;
```

```
entity ff_d is  
  port ( d, clock: in std_logic;  
         q, qn: out std_logic);  
end ff_d;
```
 
```
architecture bhv of ff_d is  
  signal qt,qnt: std_logic;  
begin  
  process (d,clock)  
  begin  
    if (clock'event and clock='1') then  
      qt<=d;  
    end if;  
  end process;  
  q <= qt; qn <= not(qt);  
end bhv;
```




Finite State Machine

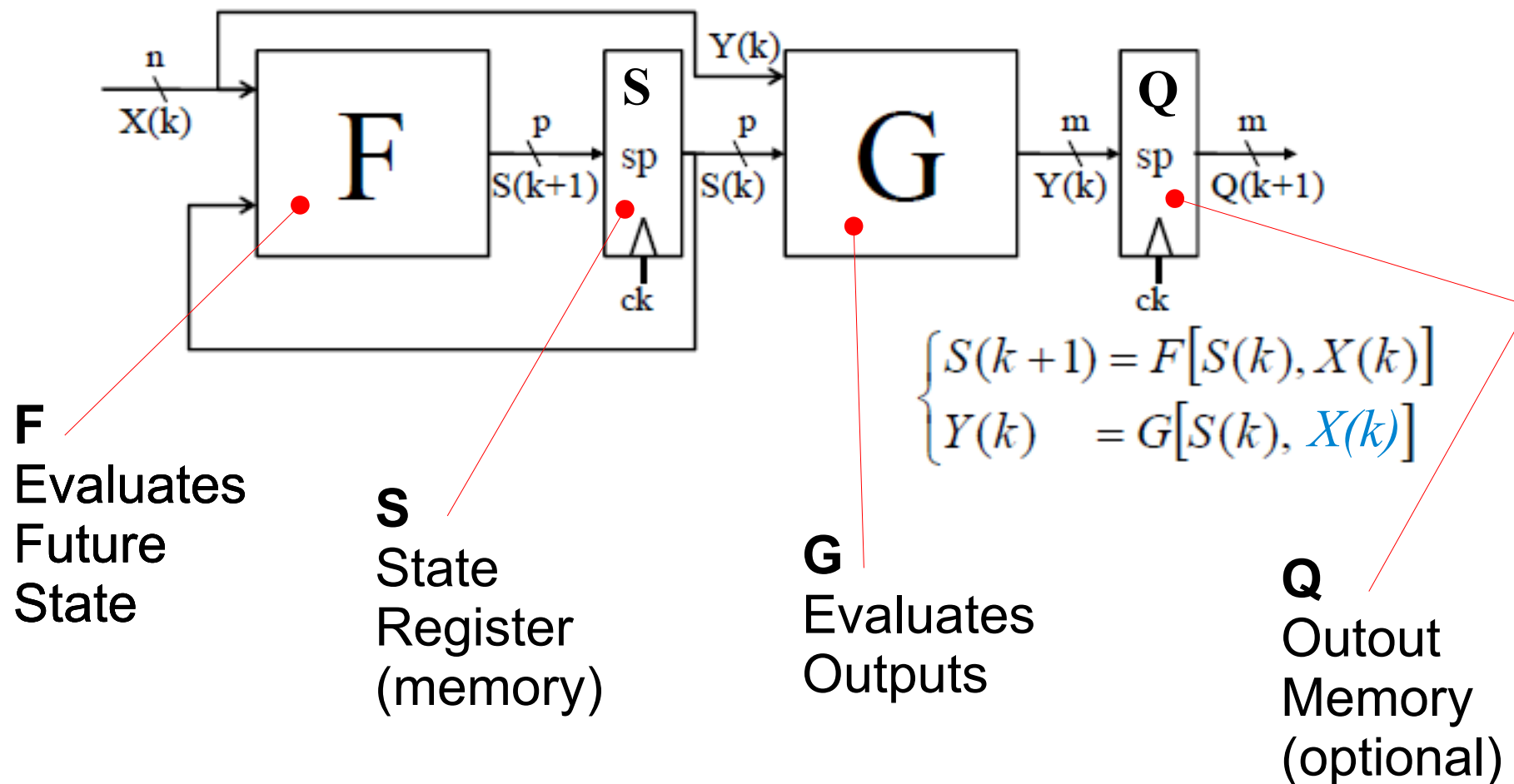

Various model options:

- 2 combinatorial (F,G) + 2 clock driven processes (S,Q)
- 2 processes: clock driven (F+S) + combinatorial (G)
- 2 processes: combinatorial (F+G) + clock driven (S+Q)

Finite State Machine

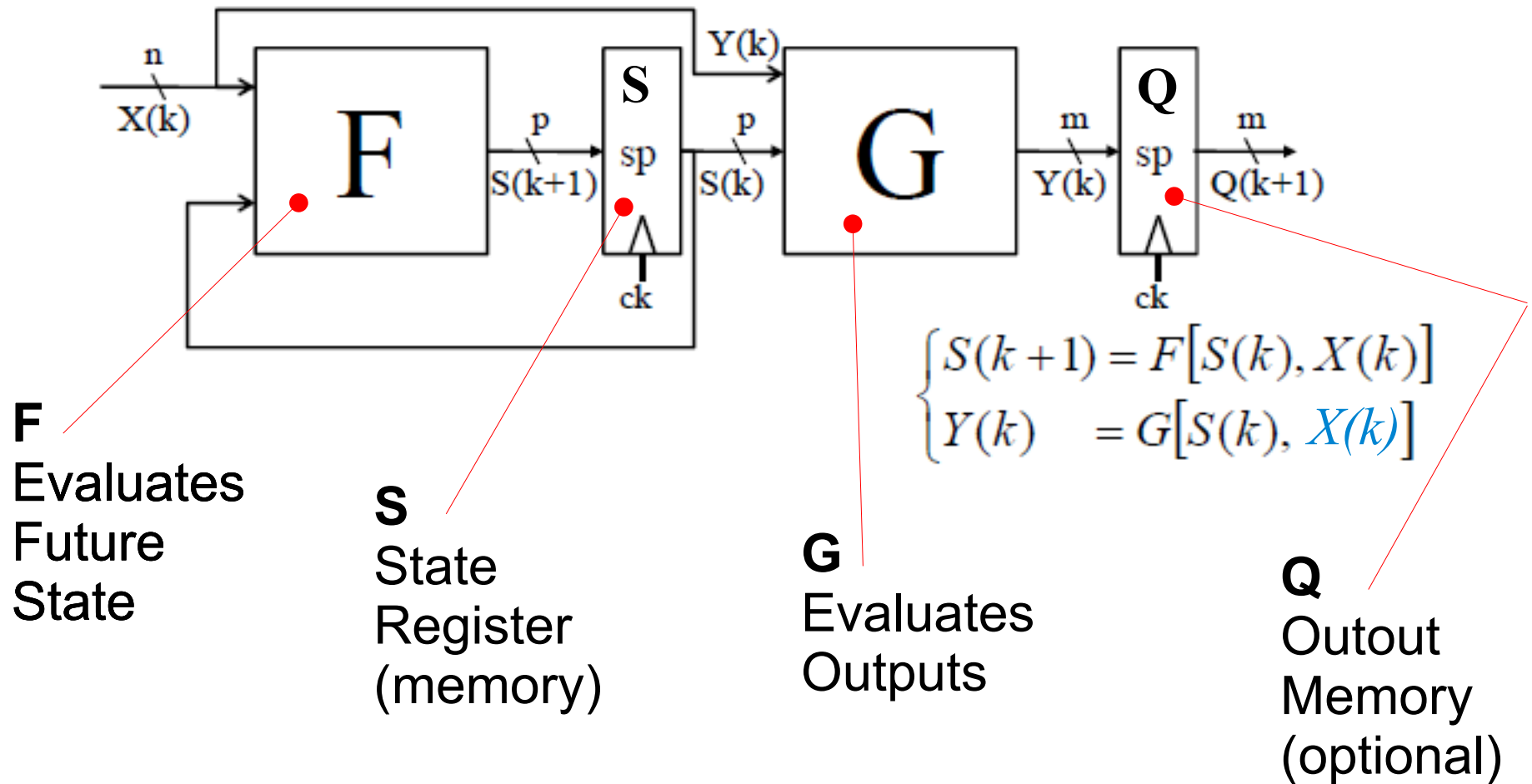


Descriptions

- X, Y, Q usually \rightarrow `std_logic_vector`
- S states \rightarrow ad hoc `enumeration` type (synthesis tool)


Example of FSM: 2-bit counter

- Moore type FSM
- Functional descr: $\text{COUNT} = 00 \rightarrow 01 \rightarrow 10 \rightarrow 11 \rightarrow 00 \rightarrow \dots$

Block
description

 


Functional description

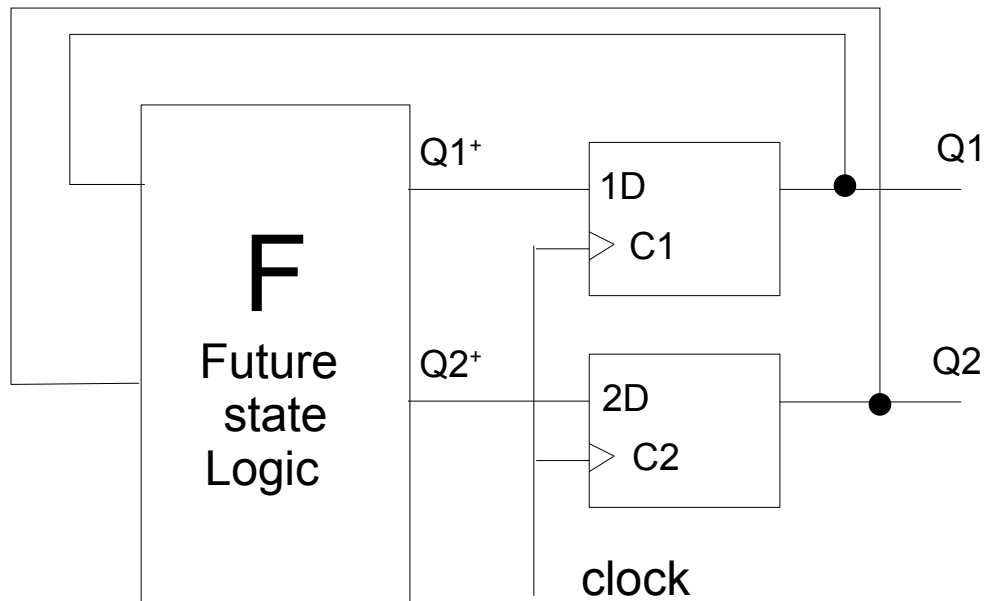

Example of FSM: 2-bit counter

- Moore type FSM
- Functional descr: $\text{COUNT} = 00 \rightarrow 01 \rightarrow 10 \rightarrow 11 \rightarrow 00 \rightarrow \dots$

Block
description

 


Truth Table description

Q2 Q1	Q2 ⁺ Q1 ⁺
0 0	0 1
0 1	1 0
1 0	1 1
1 1	0 0

$Q1^+ = \text{NOT } Q1$
 $Q2^+ = Q1 \text{ XOR } Q2$


Circuit description

 


Example of FSM: 2-bit counter

- Moore type FSM
- Functional descr: $\text{COUNT} = 00 \rightarrow 01 \rightarrow 10 \rightarrow 11 \rightarrow 00 \rightarrow \dots$

Block
description

 

Graph type
description

 

→ Algorithmic
type description:
very useful starting point for generic FSM sythesis

Example of FSM: 2-bit counter

- Moore type FSM
- Functional descr: COUNT = 00 → 01 → 10 → 11 → 00 → ...

VHDL description

```
library ieee;  
use ieee.std_logic_1164.all;
```

```
entity my_2bitcounter is  
    port ( clock, resetn: in std_logic;  
          Q: out std_logic_vector (1 downto 0));  
end my_2bitcounter;
```

```
architecture bhv of my_2bitcounter is
```

```
    type state is (S1,S2,S3,S4);  
    signal y: state;
```

custom definition of signal y
as ad hoc type state with 4
possible values (S1, ..., S4)

```
begin
```



```
    Transitions: process (resetn, clock)
```

```
    begin
```

```
        if resetn = '0' then -- asynchronous signal  
            y <= S1; -- initial state
```

```
...
```

Entity description

  

process defining the
state transition

Example of FSM: 2-bit counter

```
Transitions: process (resetn, clock)
begin
    if resetn = '0' then -- asynchronous signal
        y <= S1; -- initial state
    elsif (clock'event and clock='1') then
        case y is
            when S1 => y <= S2;
            when S2 => y <= S3;
            when S3 => y <= S4;
            when S4 => y <= S1;
        end case;
    end if;
end process;
```

Process defining the
state transitions

Note: transitions
only occur on the rising
edge

```
Outputs: process (y)
begin
    case y is
        when S1 => Q <= "00";
        when S2 => Q <= "01";
        when S3 => Q <= "10";
        when S4 => Q <= "11";
    end case;
end process;
end bhv;
```

Process defining the
outputs

Note 1) the output is not controlled by
the clock edge



Note 2) the outputs only depend on the
current state

→ Moore type FSM

Example of FSM: BCD counter w/ stop signal

- Moore-type FSM
- If the 'stop' signal is asserted, the count stops. If 'stop' is not asserted, the count continues.

BCD = Binary Coded Decimal

  

Example of FSM: BCD counter w/ stop signal

```
library ieee;  
use ieee.std_logic_1164.all;
```

VHDL description

```
entity bcd_count is  
  port ( clock, resetn, stop: in std_logic;  
        Q: out std_logic_vector (3 downto 0) );  
end bcd_count;
```

```
architecture bhv of bcd_count is
```

Custom datatype definition: 'state'
with 10 possible values: S1 to S10

```
type state is (S1,S2,S3,S4,S5,S6,S7,S8,S9,S10);
```

```
signal y: state;
```

Definition of signal 'y' of type 'state'.

```
begin
```

```
Transitions: process (resetn, clock, stop)  
begin
```

```
  if resetn = '0' then -- asynchronous signal  
    y <= S1; -- initial state
```

Process that
defines the
state transitions

```
...
```

Example of FSM: BCD counter w/ stop signal

```
...
elsif (clock'event and clock='1') then
  case y is
    when S1 =>
      if stop='1' then y<=S1; else y<=S2; end if;
    when S2 =>
      if stop='1' then y<=S2; else y<=S3; end if;
    when S3 =>
      if stop='1' then y<=S3; else y<=S4; end if;
    when S4 =>
      if stop='1' then y<=S4; else y<=S5; end if;
    when S5 =>
      if stop='1' then y<=S5; else y<=S6; end if;
    when S6 =>
      if stop='1' then y<=S6; else y<=S7; end if;
    when S7 =>
      if stop='1' then y<=S7; else y<=S8; end if;
    when S8 =>
      if stop='1' then y<=S8; else y<=S9; end if;
    when S9 =>
      if stop='1' then y<=S9; else y<=S10; end if;
    when S10 =>
      if stop='1' then y<=S10; else y<=S1; end if;
  end case;
end if;
end process;
...
```


Note that the state transitions depend on the stop signal 'stop'

Process that defines the state transitions

Note that the state transitions only occur on the rising clock edge

 Example of FSM: BCD counter w/ stop signal

```
...  
Outputs: process (y)  
begin  
    case y is  
        when S1 => Q <= "0000";  
        when S2 => Q <= "0001";  
        when S3 => Q <= "0010";  
        when S4 => Q <= "0011";  
        when S5 => Q <= "0100";  
        when S6 => Q <= "0101";  
        when S7 => Q <= "0110";  
        when S8 => Q <= "0111";  
        when S9 => Q <= "1000";  
        when S10 => Q <= "1001";  
    end case;  
end process;  
end bhv;
```





Note that the outputs only depend on the current state, hence this is a Moore machine

Process that defines the outputs

Note that the output is not controlled by the rising clock edge, only by the current state.

 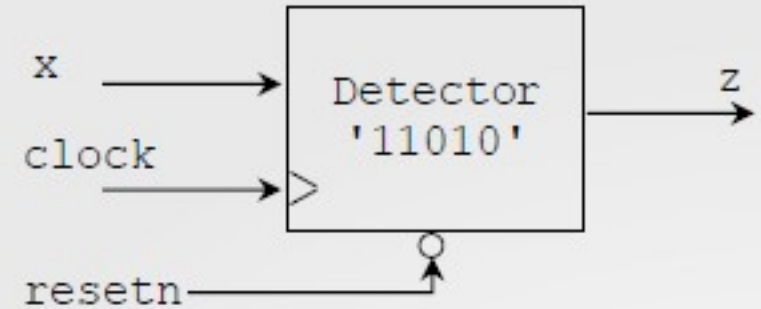Example of FSM: sequence detector w/ overlap

- Mealy-type FSM
- It detects the sequence 11010
- State Diagram: 5 states



Example of FSM: sequence detector w/ overlap

▪ VHDL Code: Mealy FSM

```
library ieee;  
use ieee.std_logic_1164.all;
```

```
entity my_seq_detect is  
  port ( clock, resetn, x: in std_logic;  
        z: out std_logic);  
end my_seq_detect;
```


```
architecture bhv of my_seq_detect is
```

```
  type state is (S1,S2,S3,S4,S5);
```

```
  signal y: state;
```

```
begin
```
 
```
  Transitions: process (resetn, clock, x)  
  begin  
    if resetn = '0' then -- asynchronous signal  
      y <= S1; -- initial state
```




Custom datatype definition: 'state'
with 5 possible values: S1 to S5

Definition of signal 'y' of type 'state'.

Process that
defines the state
transitions

Example of FSM: sequence detector w/ overlap

■ VHDL Code: Mealy FSM

 

```
...  
    elsif (clock'event and clock='1') then
```

```
        case y is
```

```
            when S1 =>
```

```
                if x = '1' then y<=S2; else y<=S1; end if;
```

```
            when S2 =>
```

```
                if x = '1' then y<=S3; else y<=S1; end if;
```

```
            when S3 =>
```

```
                if x = '1' then y<=S3; else y<=S4; end if;
```

```
            when S4 =>
```

```
                if x = '1' then y<=S5; else y<=S1; end if;
```

```
            when S5 =>
```

```
                if x = '1' then y<=S3; else y<=S1; end if;
```

```
        end case;
```

```
    end if;
```

```
end process;
```

```
...
```

Note that the state transitions depend on the input signal 'x'

Process that defines the state transitions


Note that the state transitions only occur on the rising clock edge

Example of FSM: sequence detector w/ overlap

■ VHDL Code: Mealy FSM

...
 
```
Outputs: process (x,y)
begin
  z <= '0';
  case y is
    when S1 =>
    when S2 =>
    when S3 =>
    when S4 =>
    when S5 =>
      if x = '0' then z <= '1'; end if;
  end case;
end process;
end bhv;
```




Note that the output depends on the current state and the input 'x', hence this is a Mealy machine.



Process that defines the outputs

Algorithmic State Machine (ASM) representation

 
- This is an efficient way to represent Finite State Machines.
- We use the 11010 detector as an example here.



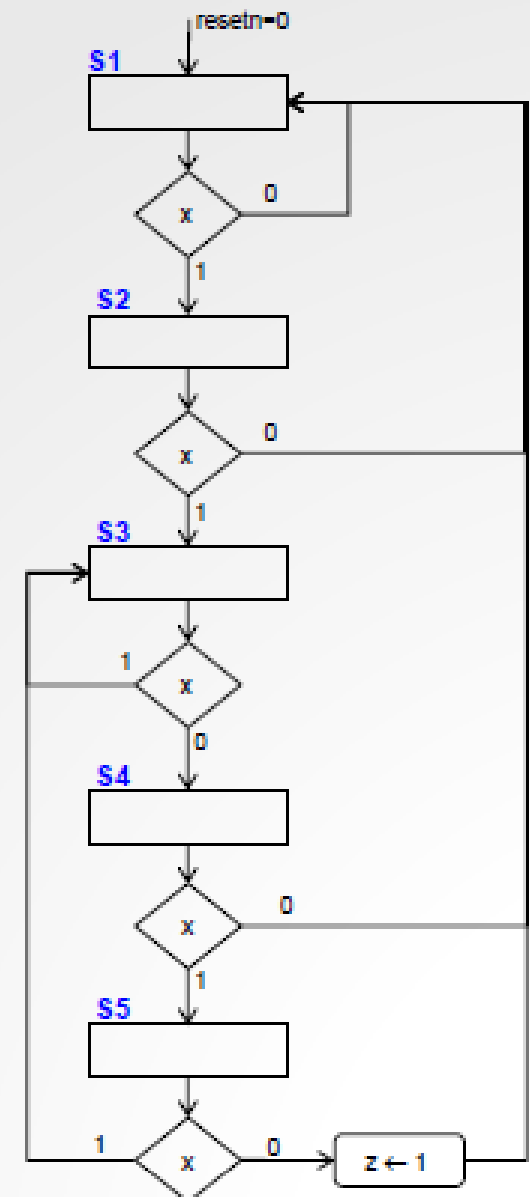 Starting points for building the VHDL description



FMS models

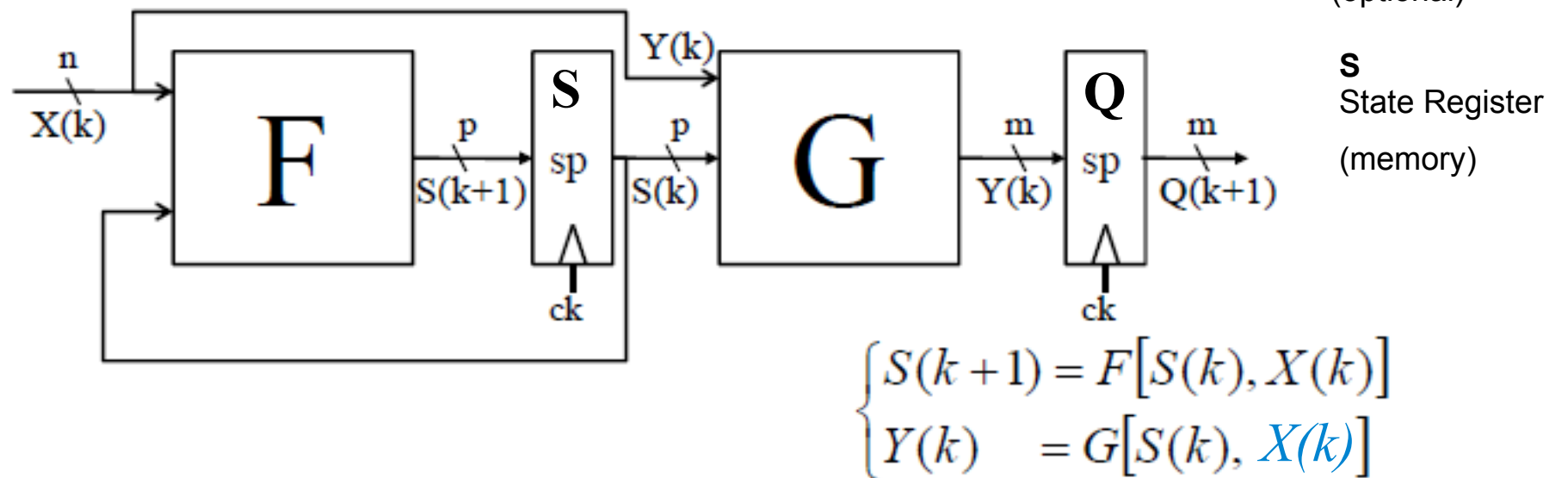

Various model options:

- 2 combinatorial (F,G) + 2 clock driven processes (S,Q)

• 2 processes: clock driven (F+S) + combinatorial (G)

- 2 processes: combinatorial (F+G) + clock driven (S+Q)

up to now this was the model, let's check alternative

FMS – sequence detector “1101”

Mealy type

```
library IEEE;  
use IEEE.STD_LOGIC_1164.all;
```

```
entity MSF1 is  
port(MSF_IN, CK, R: in std_logic;  
MSF_OUT: out std_logic);  
end MSF1;
```

```
architecture RTL of MSF1 is
```


```
-- STATO e` un'enumerazione; i dati di tipo STATO possono  
-- assumere solo i valori A, B, C, D. I due segnali stato_pres  
-- e stato_fut sono dichiarati di questo tipo
```

```
type STATO is (A, B, C, D);  
signal STATO_PRE, STATO_FUT: STATO := A;  
signal Y: std_logic;
```

```
begin
```

```
-- Il processo P1 modella le funzioni F e G della macchina,  
-- quindi si attiva quando c'e` un evento su STATO_PRE o  
-- sul segnale di ingresso MSF_IN
```
 
```
P1: PROCESS(STATO_PRE, MSF_IN)  
STATO_PRE, MSF_IN)  
begin
```



Process P1
modeling
F and G

FMS – sequence detector “1101”

```
-- le funzioni F e G sono
-- descritte con istruzioni
-- case e if...then...else
case STATO_PRES is
  when A =>
    if MSF_IN = '0' then
      STATO_FUT <= A;
      Y <= '0';
    else
      STATO_FUT <= B;
      Y <= '0';
    end if;
  when B =>
    if MSF_IN = '0' then
      STATO_FUT <= A;
      Y <= '0';
    else
      STATO_FUT <= C;
      Y <= '0';
    end if;
```

```
when C =>
  if MSF_IN = '0' then
    STATO_FUT <= D;
    Y <= '0';
  else
    STATO_FUT <= C;
    Y <= '0';
  end if;
when D =>
  if MSF_IN = '0' then
    STATO_FUT <= A;
    Y <= '0';
  else
    STATO_FUT <= A;
    Y <= '1';
  end if;
end case;
end process P1;
-- continua
```

FMS – sequence detector “1101”

```
-- Il processo P2 modella i
-- registri della macchina
P2: process(CK)
begin
    if CK'event and CK = '1' then
        if R = '0' then
            STATO_PRES <= A;
            MSF_OUT <= '0';
        else
-- STATO_FUT proviene dal
-- dal processo P1
            STATO_PRES <= STATO_FUT;
-- il registro di uscita è
-- opzionale; elimina i glitch ma
-- ritarda di un ciclo l'uscita
            MSF_OUT <= Y;
        end if;
    end if;
end process P2;
end architecture rtl;
```

Process P2
modeling
S and Q

Note: Q register
useful against glitches
but
result in delayed
output

FMS – sequence detector “1101”

Moore
alternative

An alternative Moore type model consists in exploiting the state signal for representing/ encoding also the output (Then the output logic G is no more necessary just Q is needed)



output = state

Description: start from Mealy model and split A state into
- A0 (transition from D when MSF_IN=0) and
- A1 (from D when MSF_IN=1)

Output coding:

Y=0 for states A0, B, C, D

Y=1 for state A1

→ sequence: **A0:000 B:001 C:010 D:011 A1:111**

... MSB is the output Y bit

FMS – sequence detector “1101”

Moore
alternative

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
entity MSF1 is
    port(MSF_IN, CK, R: in
         std_logic;
         MSF_OUT: out std_logic);
end MSF1;
architecture RTL of MSF1 is
    type STATO is (A0,A1,B,C,D);
    attribute ENUM_ENCODING: STRING;
    attribute ENUM_ENCODING of STATO:
        type is "000 111 001 010 011";
    signal STATO_PRES, STATO_FUT:
        STATO := A0;
    signal Y: std_logic;
begin
```

```
    P1: PROCESS(STATO_PRES, MSF_IN)
    begin
        case STATO_PRES is
            when A0 =>
                Y <= '0';
                if MSF_IN = '0' then
                    STATO_FUT <= A0;
                else
                    STATO_FUT <= B;
                end if;
            end if;
```

```
        P2: process(CK)
        begin
            if CK'event and CK = '1' then
                if R = '0' then
                    STATO_PRES <= A0;
                    MSF_OUT <= '0';
                else
                    STATO_PRES <= STATO_FUT;
                    MSF_OUT <= Y;
                end if;
            end if;
        end process P2;
    end architecture rtl;
```

```
        when A1 =>
            Y <= '1';
            if MSF_IN = '0' then
                STATO_FUT <= A0;
            else
                STATO_FUT <= B;
            end if;
        when B =>
            Y <= '0';
            ...
        when D =>
            Y <= '0';
            if MSF_IN = '0' then
                STATO_FUT <= A0;
            else
                STATO_FUT <= A1;
            end if;
        end case;
    end process P1;
```


Process P2
modeling Q

Process P1
modeling
F and S

Notes: State Machines - synchronization

Edge-triggered flip-flops, synchronous counters, and shift registers are simple examples of **state machines** → which are **synchronous systems** that consist only of **edge-triggered flip-flops** and **combinational circuits**

- The **inputs** to the flip-flops in a state machine are logical functions only of the **external inputs** (if any) and of the **outputs** of the flip-flops themselves
External inputs are assumed to be **synchronized** to the system clock
- The **state of the machine between clock transitions** is completely determined by the state of the flip-flops. In any given state the **next state** is decided by the combinational logic
- One orderly way of describing a state machine is a **state diagram**, in which the **states are nodes** and the **transitions** between states are indicated by directed traces labeled with the conditions that enable these transitions.

 

Example :

state diagram of a JK flip-flop

The two states are labeled according to the value of Q

If $Q=0$, Q will remain at 0 if $J=0$, and it will go to 1 if $J=1$

If $Q=1$, Q will remain at 1 if $K=0$, and it will go to 0 if $K=1$

Notes: State Machines – robust againsts races

1) state machines are **insensitive to races** in their combinational logic because **races can occur only between clock transitions**

Example: in the shift register D3 will exhibit a short pulse if S/L goes 1→0 when DP3 and DH are both 1; but S/L is synchronized to the clock and can thus change only immediately after a clock transition, so that the pulse has no effect on Q3

2) state machines show **reduced sensitivity to inductively or capacitively coupled transients** generated by changes of state, due to the fact that **outputs change well after the decision to change is firm**


This advantage is particularly valuable when changes of state trigger high-power circuits and there are inputs connected to the outside world by long unshielded lines

Notes: State Machines – excess states

A state machine with N flip-flops has 2^N possible states → state machines generally have **more states than are needed for a given task**

Excess states → consideration of what action to take if the machine falls into one of these states (either at power-up or because of noise)

Example: the divide-by-6 Johnson counter

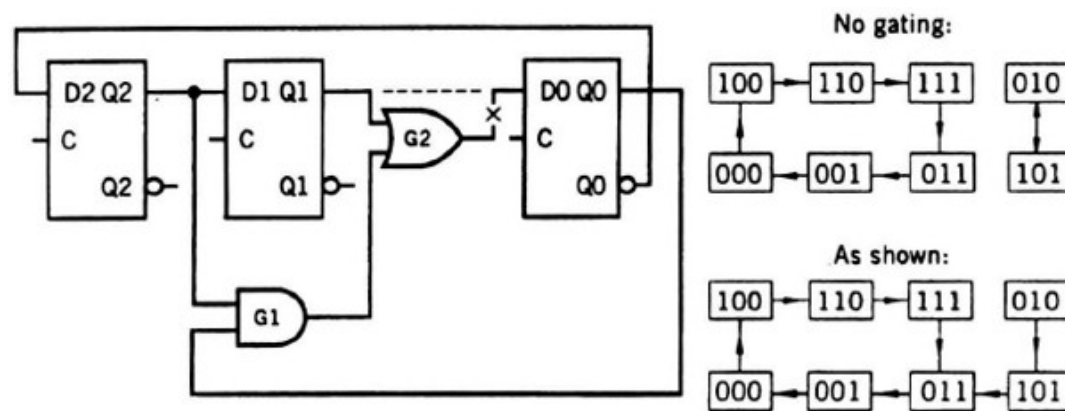

The counter has three flip-flops
→ eight possible states

The normal sequence is
000, 100, 110, 111, 011, 001, 000
and so on


In the **absence of gating**, (that is if G2 is removed and Q1 is connected to D0) states 010 and 101 form a disjoint group
→ to avoid this possibility, G1 detects state 101 and makes D0 equal to 1, thus simulating state 111 and forcing the counter into state 011

Synchronizers → for Async FSM

External inputs to state machines are assumed to be synchronous...
... but **asynchronous inputs** do exist (except in the rarest of cases)
→ must somehow be **converted into synchronous versions**

 Example: the “standard synchronizer”

Asynchronous input ASYN drives the D input of a D flip-flop
→ a change of state in D is synchronously reflected at output SYN at the first following clock transition




Note: there exists a chance of synchronization failure (as in RS flip-flops)
ie a change in ASYN might violate setup or hold requirements
→ the **flip-flop becomes metastable**


Synchronizers – failure and fundamental rule

There are several procedures to **reduce the probability P of synchronization failure**: of which we will mention only two; both result in a longer response time to ASYN

 (1) driving the standard synchronizer with a **submultiple f/N of the clock frequency f**
→ the frequency at which ASYN is sampled (and thus P) is reduced by a factor N



 (2) a much more effective procedure is illustrated by the **two-stage synchronizer**
Both ASYN and the intermediate output SYN? are sampled at a frequency f/N
→ this allows a time $T = N/f$ for SYN? to stabilize before it is copied to SYN
Since P decreases exponentially with T , it can be reduced by orders of magnitude beyond a factor N



Note: a fundamental rule about synchronization is that it must be done only once for a given asynchronous input because **different synchronizers might arrive at different decisions** even in the case that they do not become metastable:

Example: an otherwise acceptable clock skew might make one synchronizer recognize a change that another synchronizer ignores

Additional material